

PART 1 - DC CIRCUITS


DC (1)

CHARGE q AND CURRENT $i = \frac{dq}{dt}$

ALSO CALLED A
"ONE-PORT"

IN A TWO-TERMINAL DEVICE

FIG. 1

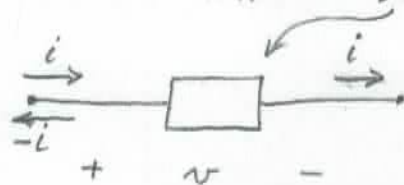

(- (-v) +)

$q = q(t)$
AND
 $i = i(t)$
CAN VARY WITH
TIME t .

CHARGE q IS THE AMOUNT OF ELECTRIC QUANTITY
MEASURED IN UNITS
OF COULOMBS
(CHARGE OF 1 ELECTRON)
 $= 1.602 \times 10^{-19}$ COULOMBS

CURRENT i IS THE FLOW OF ELECTRIC CHARGE ALONG
A WIRE - OR THROUGH THE DEVICE.

$$i = \frac{dq}{dt} \text{ AMPERES } (= \text{COULOMBS/SECOND})$$

TOTAL CHARGE FLOWING THROUGH THE DEVICE IN THE
TIME INTERVAL t_0 TO t_1 IS

$$q(t) - q(t_0) = \int_{t_0}^{t_1} i(x) dx \quad [t_1 > t_0]$$

VOLTAGE v IS THE FORCE PRODUCING THE CURRENT i ,
 $v = v(t)$ IS MEASURED IN VOLTS.

SO THE POWER p PRODUCED AT ANY INSTANT OF TIME t IS

$$p = vi \quad \text{OR} \quad p(t) = v(t)i(t).$$

p IS MEASURED IN WATTS W AND IS POWER DISSIPATED
WHEN v AND i HAVE THE POLARITIES OF FIG.

SO, THE TOTAL ENERGY E PRODUCED BY p DURING t_0 TO t_1 ,
($t_1 > t_0$)

$$E(t_0, t_1) = \int_{t_0}^{t_1} v(x) i(x) dx = \int_{t_0}^{t_1} p(x) dx$$

E IS MEASURED IN UNITS OF JOULES

$$\text{THUS, } \frac{1 \text{ JOULE}}{1 \text{ SECOND}} = 1 \text{ WATT.}$$

IF $v(-\infty) = i(-\infty) = 0$, THEN.

$$E(-\infty, t) = \int_{-\infty}^t v(x) i(x) dx = \int_{-\infty}^t p(x) dx$$

A PASSIVE ONE-PORT IS A ONE-PORT SUCH THAT

$$E(-\infty, t) = \int_{-\infty}^t p(x) dx \geq 0 \quad \text{FOR ALL } t.$$

AN ACTIVE ONE-PORT IS A ONE-PORT FOR WHICH

$$E(-\infty, t) < 0 \quad \text{AT SOME } t \text{ AND FOR SOME } v(t).$$


(AN ACTIVE ONE-PORT HAS A SOURCE OF ELECTRICAL ENERGY
 WITHIN IT --- SUCH AS A BATTERY.)

TWO IMPORTANT ACTIVE ONE-PORT


1. THE INDEPENDENT VOLTAGE SOURCE:

HERE, $e(t) = -v(t)$ IS SPECIFIED AND IS UNAFFECTED BY $i(t)$.

By (11)

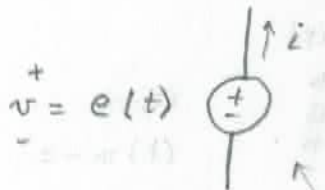


SPECIAL CASE: THE IDEAL BATTERY

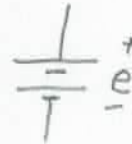

SO, IN A PLOT OF v VERSUS i WE HAVE:

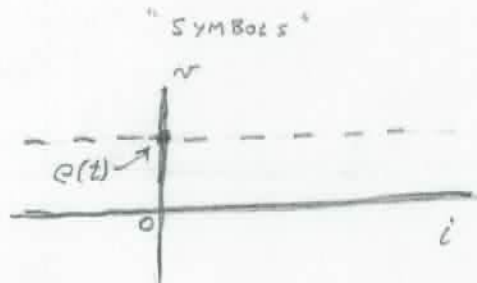$e(t)$ CAN VARY UP AND DOWN WITH RESPECT TO t .




NOTE. v IS NOW TAKEN WITH A POLARITY OPPOSITE TO THAT OF FIG. 1

NOW, $v = e(t)$ IS MEASURED AS A VOLTAGE RISE WITH RESPECT TO DIRECTION OF CURRENT i .

SO, IF $i(t) > 0$ AND $e(t) > 0$ AT SOME t ,


WE GET POWER GENERATED (RATHER THAN DISSIPATED).

2. THE INDEPENDENT CURRENT SOURCE:

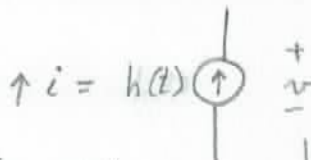

So now:

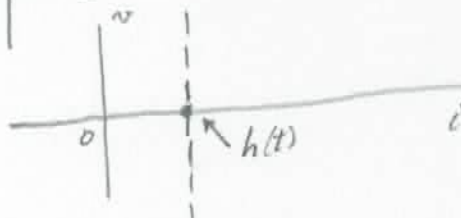$h(t)$ CAN VARY LEFT AND RIGHT WITH RESPECT TO t .



NOTE. i IS NOW TAKEN WITH A POLARITY OPPOSITE TO THAT OF FIG. 1

SO, IF $v(t) > 0$ AND $h(t) > 0$ AT SOME t ,


WE AGAIN GET POWER GENERATED (RATHER THAN DISSIPATED).

(NOTE. CURRENT SOURCES ARE UNUSUAL, IN CONTRAST TO VOLTAGE SOURCES.)


RESISTORS R (SYNONYMOUSLY, RESISTANCES)

OHM'S LAW: $v(t) = R i(t)$, WHERE R IS A CONSTANT
 USUALLY POSITIVE.


Fig. 2

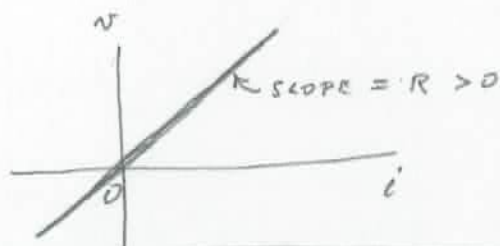

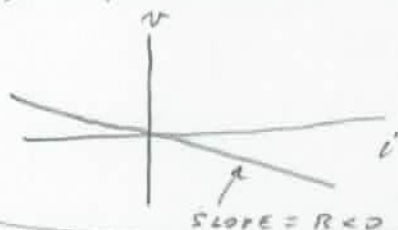
WE COULD ALSO HAVE A NEGATIVE RESISTOR $R < 0$



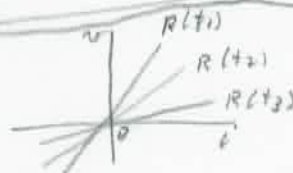WE COULD ALSO HAVE A TIME-VARYING RESISTOR:



OR A NONLINEAR RESISTOR:

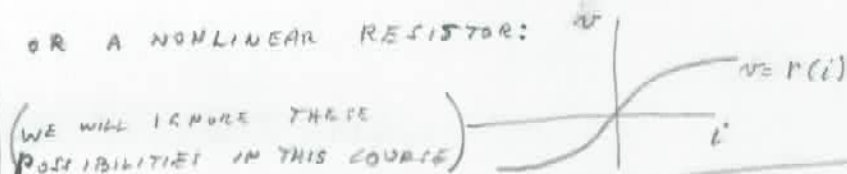UNITS

$$v \text{ (IN VOLTS V)} = R \text{ (IN OHMS } \Omega) i \text{ (IN AMPERES A)}$$

$$(V = \Omega A)$$

FOR A FIXED (I.E., CONSTANT) RESISTOR R , POWER DISSIPATED (SEE POLARITIES OF FIG. 2)

$$p(t) = v(t) i(t) = R(i(t))^2 = \frac{(v(t))^2}{R}$$

IS:

$$\text{FOR } R > 0, R \text{ IS PASSIVE: } E(t) = \int_{-\infty}^t p(x) dx = \int_{-\infty}^t R(i(x))^2 dx \geq 0$$

CONDUCTANCE G IS THE RECIPROCAL OF RESISTANCE R :

$$G = \frac{1}{R} \quad (\text{UNITS SIEMENS} = \frac{1}{\text{OHMS}})$$

SIEMENS = MHOS
 OLDER NAME


$$\text{THUS, } i(t) = G v(t)$$

$$p(t) = \frac{i(t)^2}{G} = G v(t)^2$$

KIRCHOFF'S LAWS

DC (5)

A "NETWORK" →

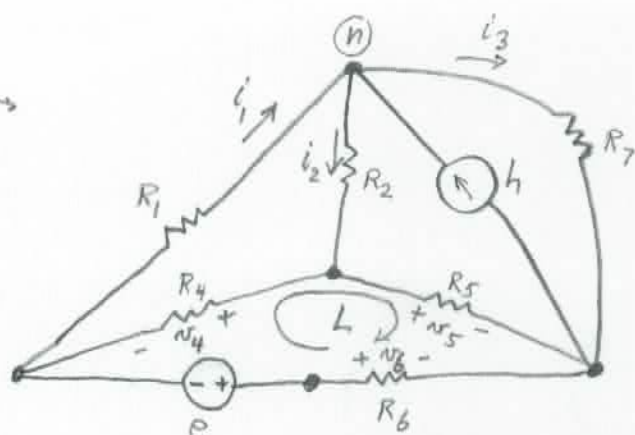

A NODE IS WHERE LINES MEET. (EXAMPLE: n)

A BRANCH IS AN ELEMENT BETWEEN ADJACENT NODES.

A LOOP IS A TRACING THROUGH THE NETWORK THAT ENDS AT THE NODE WHERE IT STARTED. (EXAMPLE: L)

A MESH IS A SPECIAL CASE OF A LOOP (TO BE EXPLAINED)

KIRCHHOFF'S CURRENT LAW (KCL):

THE "ALGEBRAIC SUM" OF ALL CURRENTS FLOWING IN TOWARD A NODE EQUALS 0.

EXAMPLE: AT NODE (n): $i_1 - i_2 + h - i_3 = 0$

(A GENERALIZATION: THE ALGEBRAIC SUM OF ALL CURRENT ENTERING A CLOSED SURFACE EQUALS 0.)

KIRCHOFF'S VOLTAGE LAW (KVL):

THE "ALGEBRAIC SUM" OF ALL VOLTAGE DROPS AROUND ANY LOOP EQUALS 0.

EXAMPLE: AROUND LOOP L (TRACING CLOCKWISE):

$$-v_4 + v_5 - v_6 + E = 0$$

A BASIC FACT:


OHM'S LAW + KVL + KCL DETERMINE ALL THE CURRENTS AND VOLTAGES IN THE NETWORK (N=RI)

(BUT THERE ARE UNUSUAL EXCEPTIONS).

SERIES RESISTANCE AND VOLTAGE DIVISION

A SERIES CIRCUIT OCCURS WHEN EVERY NODE - EXCEPT FOR POSSIBLY THE TWO END NODES -


HAVE EXACTLY 2 BRANCHES CONNECTED TO IT.

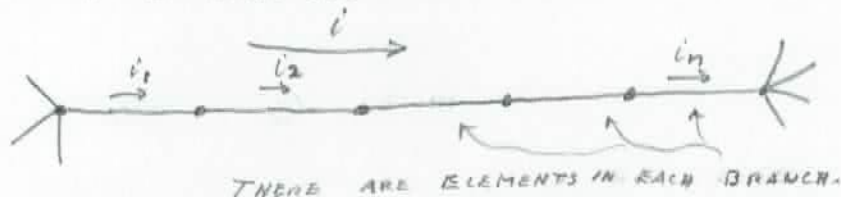

BECAUSE OF KCL: THE CURRENTS IN EACH BRANCH ARE ALL THE SAME

$$i_1 = i_2 = \dots = i_n = i$$

A PARTICULAR CASE:

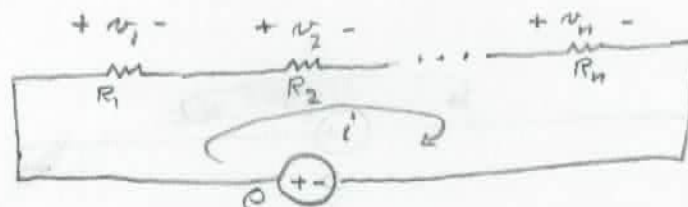

KVL: $e = v_1 + v_2 + \dots + v_n$

OHM'S LAW: $v_1 = R_1 i, \dots, v_n = R_n i$

THUS, $e = R_1 i + \dots + R_n i = (R_1 + \dots + R_n) i$

SET $R_s = R_1 + \dots + R_n$


R_s = EQUIVALENT RESISTANCE OF THE SERIES CIRCUIT OF RESISTORS

SO, $i = \frac{e}{R_s}$ AND $v_1 = \frac{R_1}{R_s} e, \dots, v_n = \frac{R_n}{R_s} e$.

THESE ARE THE "VOLTAGE DIVISION" EQUATIONS.

THAT IS, THE TOTAL VOLTAGE e SPLITS UP ALONG THE RESISTORS R_k ($k=1, \dots, n$) IN PROPORTION TO THOSE RESISTORS R_k .

EXAMPLE:

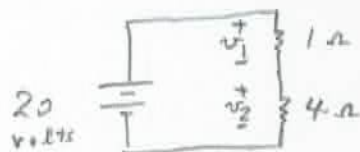

$$v_1 = \frac{1}{5} \times 20 = 4 \text{ volts}$$

$$v_2 = \frac{4}{5} \times 20 = 16 \text{ volts}$$

LET'S ADD UP ALL THE POWERS DISSIPATED IN THE RESISTORS:

$$\begin{aligned}
 P &= \frac{v_1^2}{R_1} + \dots + \frac{v_n^2}{R_n} = \frac{1}{R_1} \left(\frac{R_1}{R_s} e \right)^2 + \dots + \frac{1}{R_n} \left(\frac{R_n}{R_s} e \right)^2 \\
 &= \frac{R_1}{R_s^2} e^2 + \dots + \frac{R_n}{R_s^2} e^2 = \frac{R_1 + \dots + R_n}{R_s^2} e^2 \\
 &= \frac{R_s}{R_s^2} e^2 = \frac{e^2}{R_s} = ei = \text{POWER GENERATED BY THE SOURCE } e.
 \end{aligned}$$

THUS, WE SEE THAT THE TOTAL POWER DISSIPATED IN ALL THE RESISTORS EQUALS THE POWER GENERATED IN THE SOURCE e .

This is a general principle - called Tellegen's Theorem:


In any network of positive resistors and independent sources, the total power dissipated in the resistors equals the total power generated in all the sources.

(but some of the sources may be dissipating instead of generating.)

PARALLEL RESISTORS AND CURRENT DIVISION

(This is the "dual" of series resistors!)
 $R \rightarrow G$, $v \rightarrow i$, $i \rightarrow v$

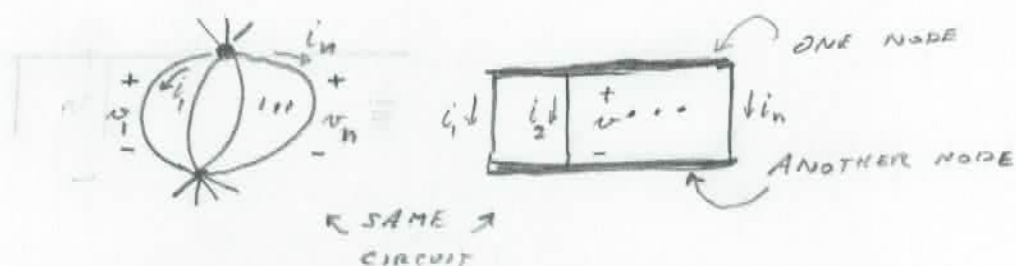A PARALLEL CIRCUIT OCCURS WHEN TWO OR MORE BRANCHES ARE CONNECTED TO THE SAME TWO NODES.




BECAUSE OF KVL: THE VOLTAGES ON EACH BRANCH ARE ALL THE SAME.

$$v_1 = v_2 = \dots = v_n = v$$

A PARTICULAR CASE:

FIG. A

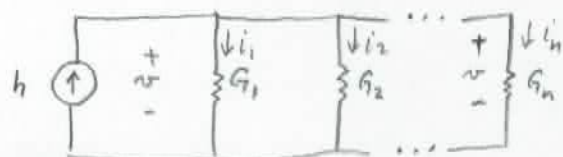

$$G_k = \frac{1}{R_k}, \quad k = 1, \dots, n.$$

KCL: $h = i_1 + i_2 + \dots + i_n$

OHM'S LAW: $i_1 = G_1 v$, \dots , $i_n = G_n v$

THUS, $h = (G_1 + \dots + G_n) v = G_p v$

SET $G_p = G_1 + \dots + G_n$

(2) \rightarrow

G_p = EQUIVALENT CONDUCTANCE OF THE PARALLEL CIRCUIT OF RESISTORS.

SO, $v = \frac{h}{G_p}$ AND $i_1 = \frac{G_1}{G_p} h$, \dots , $i_n = \frac{G_n}{G_p} h$

THESE ARE THE "CURRENT DIVISION" EQUATIONS.


THAT IS, THE TOTAL CURRENT h SPLIT UP AMONG THE CONDUCTANCES G_k IN PROPORTION WITH THOSE CONDUCTANCES.

USUALLY, WE WORK WITH RESISTANCES, (NOT CONDUCTANCES).

SO, EQUATION (2) IS ALSO GIVEN BY

$$R_p = \frac{1}{G_p} = \frac{1}{G_1 + \dots + G_n} = \frac{1}{\frac{1}{R_1} + \dots + \frac{1}{R_n}}$$

EXAMPLE: TWO RESISTORS IN PARALLEL.

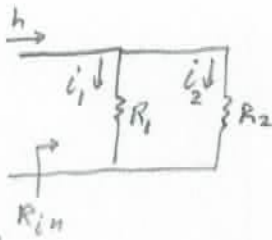

$$i_1 = \frac{G_1}{G_1 + G_2} h = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} h = \frac{R_2}{R_1 + R_2} h$$

SIMILARLY, $i_2 = \frac{R_1}{R_1 + R_2} h$

THESE EQUATIONS WORK ONLY FOR 2 RESISTORS ONLY.

FOR 3 OR MORE RESISTORS, WE HAVE TO USE

$$i_k = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \dots + \frac{1}{R_n}} h.$$

WITH REGARD TO POWER RELATIONS, WE AGAIN HAVE
 THAT THE TOTAL POWER DISSIPATED IN ALL THE RESISTORS
 EQUALS THE POWER GENERATED IN THE CURRENT SOURCE h :

SEE FIG. A:

$$i_1^2 R_1 + \dots + i_n^2 R_n = \left(\frac{G_1}{G_p} h \right)^2 R_1 + \dots + \left(\frac{G_n}{G_p} h \right)^2 R_n$$

$$= \frac{G_1}{G_p^2} h^2 + \dots + \frac{G_n}{G_p^2} h^2$$


$G_1 R_1 = 1$

$G_n R_n = 1$

$$= \frac{G_1 + \dots + G_n}{G_p^2} h^2 = \frac{h^2}{G_p} = \nu h = \text{POWER GENERATED IN THE CURRENT SOURCE } h.$$

$\frac{h}{G_p} = R_p h = \nu$

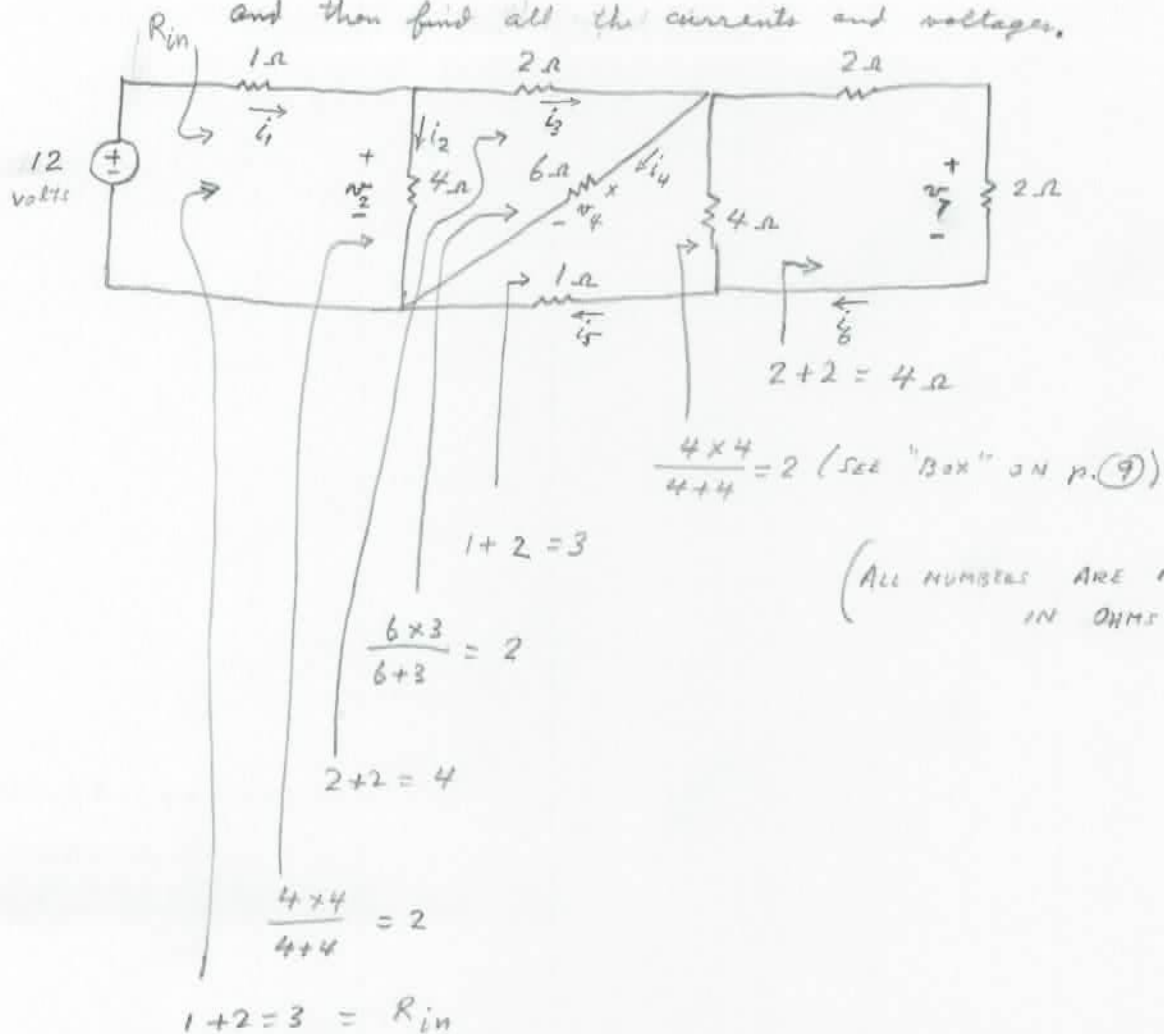Example Find the input resistance R_{in} of the following series-parallel circuit, and then find all the currents and voltages.



TO GET SOME OF THE CURRENTS AND VOLTAGES: (ALL THE OTHERS CAN BE OBTAINED SIMILARLY.)

$$i_1 = \frac{12}{R_{in}} = \frac{12}{3} = 4 \text{ A}$$

$$\text{KVL: } v_2 + 1 \times i_1 = 12, \quad v_2 = 12 - 4 = 8$$

$$\text{OHM'S LAW: } i_2 = \frac{v_2}{4} = 2 \text{ A}$$

$$\text{KCL: } i_3 = i_1 - i_2 = 4 - 2 = 2 \text{ A}$$

$$\text{KVL: } v_2 = 2i_3 + v_4, \quad 8 = 2 \times 2 + v_4, \quad v_4 = 4$$


$$\text{KCL: } i_5 + i_4 + i_2 = i_1, \quad i_5 + \frac{v_4}{6} + i_2 = i_1, \quad i_5 + \frac{4}{6} + 2 = 4, \quad i_5 = 4 - 2 - \frac{2}{3} = \frac{4}{3}$$

$$\text{CURRENT DIVISION: } i_6 = i_5 \frac{4}{4+4} = \frac{2}{3}$$

$$\text{OHM'S LAW: } v_7 = 2i_6 = \frac{4}{3} \text{ volts}$$


THEVENIN AND NORTON EQUIVALENT CIRCUITS

THEVENIN'S CIRCUIT

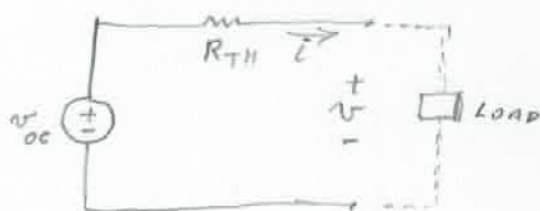

$$v = -R_{TH} i + v_{OC}$$

NORTON CIRCUIT


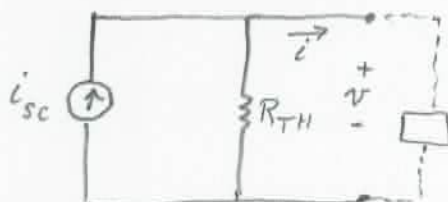


$$i_{SC} = i + \frac{v}{R_{TH}}$$

$$(OR) v = -R_{TH} i + R_{TH} i_{SC}$$

These circuits and equations are the same so far as the terminal v and i are concerned, if $v_{OC} = R_{TH} i_{SC}$.


Graphs of the equations:

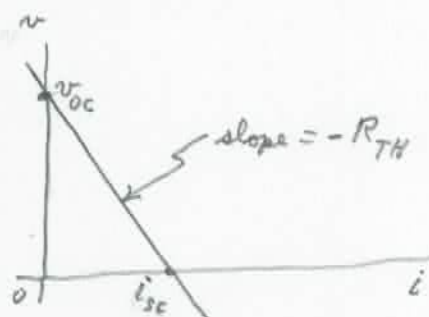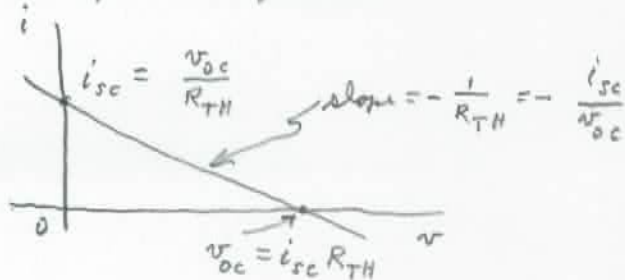

R_{TH} = INPUT RESISTANCE WHEN SOURCES ARE REMOVED.

SHORT v_{OC}
OPEN i_{SC}

A USE OF THESE CIRCUITS:

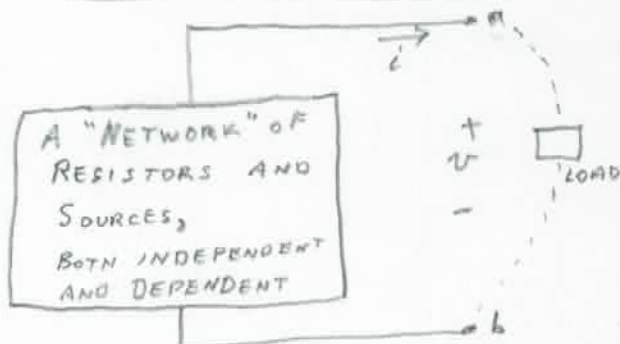

Measure v when $i = 0$. This gives $v = v_{OC}$. (open circuit at a, b.)


Measure i when $v = 0$. This gives $i = i_{SC}$. (Short circuit at a, b.)

$$\text{Set } R_{TH} = \frac{v_{OC}}{i_{SC}}$$

Then this "network" can be replaced by either Thevenin's circuit or Norton's circuit to get the same v and i at the terminals a, b whatever the load happens to be. This simplifies the calculation of v and i , as we keep changing the load.


Example: Here's another use of the equivalence of the Thevenin and Norton circuits to analyze a circuit.

Problem: Get v and i in this circuit

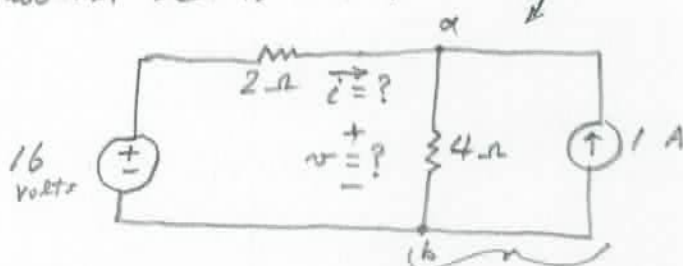


This is a Norton form of circuit: $R_{TH} = 4$, $i_{sc} = 1$ A.

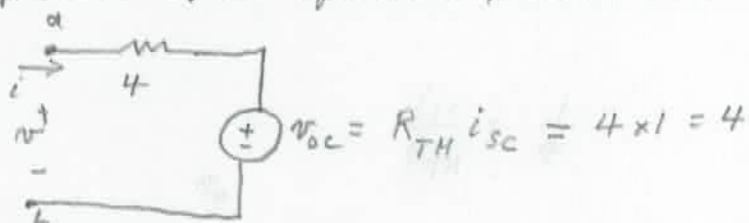Replace it by its equivalent Thevenin circuit:



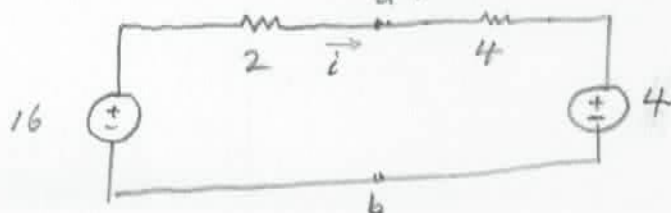So equivalently with respect to v and i , we have




Apply KVL: $-16 + 2i + 4i + 4 = 0$

$$i = \frac{16-4}{2+4} = 2 \text{ A.}$$

So,

$$v = 16 - 2i = 12 \text{ Volts}$$

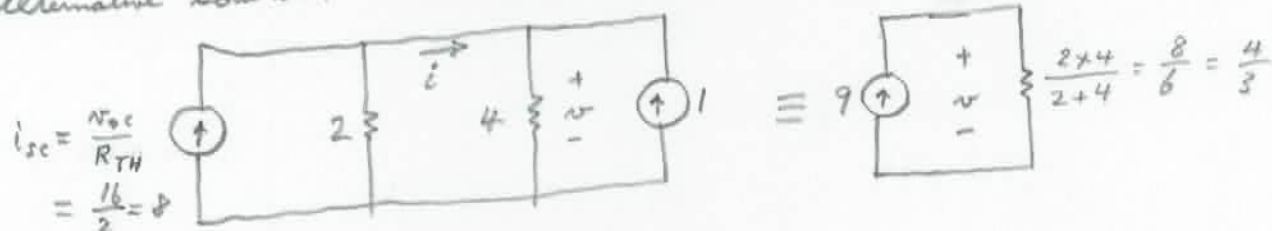Alternative solution: Use Norton's circuits:



$$v = 9 \times \frac{4}{3} = 12 \text{ Volts}$$


$$i = \frac{v}{4} - 1 = 3 - 1 = 2 \text{ A}$$

Another example

Load-line analysis for a p-n junction diode:

a "nonlinear" element


It's current-voltage curve

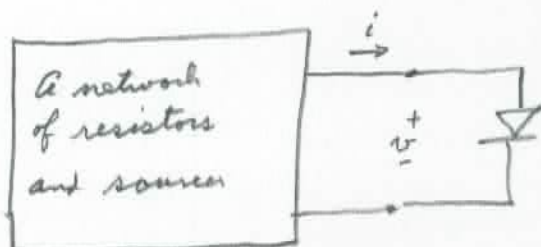Find v and i :

Use Thevenin's equivalent for this "box":



$$R_{TH} = \frac{v_{oc}}{i_{sc}}$$

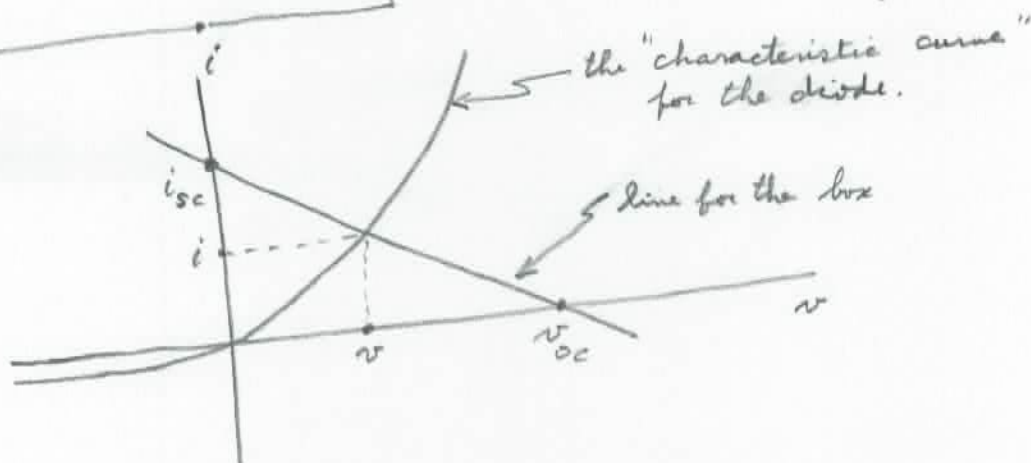


So, draw the curve for the diode,
 draw the line for the box,
 then find the point of intersection,
 \uparrow
 (i, v)

DEPENDENT SOURCES


These are very different from independent sources.

shown on page ③

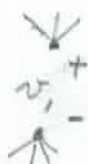VCVS = voltage-controlled voltage source:



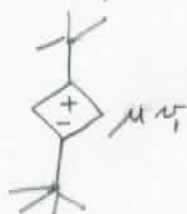Somewhere in circuit:
 v is voltage between
two nodes.



Elsewhere in circuit,

μ = constant, called
the "voltage gain."
(μ is any real number, fixed)

GCVS = current-controlled voltage source:



Somewhere:

i_1 is a current in
some branch.


Elsewhere:



$$v = r i_1$$

r = a constant, called
the "transresistance"

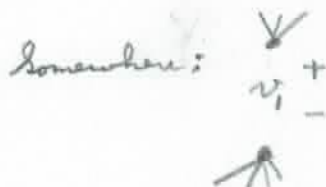VCCS = voltage-controlled current source:



Somewhere:


Elsewhere:



$$i = g v_1$$

g = a constant, called
the "transconductance"

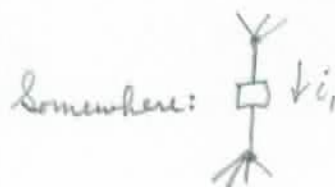CCCS = current-controlled current source:




Somewhere:

Elsewhere:



$$i = \beta i_1$$

β = a constant, called
the "current gain"

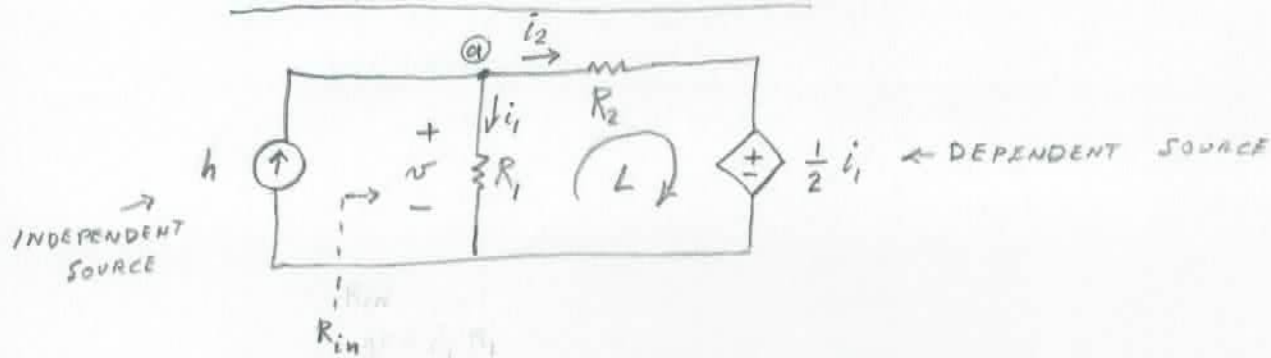AN ANALYSIS FOR A CIRCUIT:

PROBLEM: FIND i_1 , THEN FIND v , THEN FIND $R_{in} = \frac{v}{h} = \frac{v}{i_1 + i_2}$

SOLUTION: WRITE TWO EQUATIONS

① KCL AT NODE a : $-h + i_1 + i_2 = 0$

② KVL AROUND LOOP L : $-i_1 R_1 + i_2 R_2 + \frac{1}{2} i_1 = 0$

SOLVING: $i_2 = \frac{R_1 - \frac{1}{2} i_1}{R_2}$

$i_1 \left(1 + \frac{R_1 - \frac{1}{2}}{R_2}\right) = h$, so $i_1 = \frac{R_2}{R_1 + R_2 - \frac{1}{2}} h$

Don't need i_2 } \rightarrow So, $i_2 = \frac{R_1 - \frac{1}{2}}{R_2} \left(\frac{R_2}{R_1 + R_2 - \frac{1}{2}} h \right) = \frac{R_1 - \frac{1}{2}}{R_1 + R_2 - \frac{1}{2}} h$

Thus, $R_{in} = \frac{i_1 R_1}{h} = \frac{R_1 R_2}{R_1 + R_2 - \frac{1}{2}}$

Another way to get i_1 is to use matrices - see Appendix A of book.

Equations ① and ② can be written in matrix form as:

$$\begin{bmatrix} 1 & 1 \\ \frac{1}{2} - R_1 & R_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h \\ 0 \end{bmatrix}$$

Using Cramer's rule to get i_1 :

"determinants" \rightarrow $i_1 = \frac{\begin{vmatrix} h & 1 \\ 0 & R_2 \end{vmatrix}}{\begin{vmatrix} 1 & 1 \\ \frac{1}{2} - R_1 & R_2 \end{vmatrix}} = \frac{h R_2 - 0 \times 1}{R_2 - (\frac{1}{2} - R_1)} = \frac{R_2}{R_1 + R_2 - \frac{1}{2}} h$ (same answer)

Some numerical results for this example:

Let $R_1 = R_2 = 1$. We get $R_{in} = \frac{R_1 R_2}{R_1 + R_2 - \frac{1}{2}} = \frac{1}{\frac{3}{2}} = \frac{2}{3} \Omega$

↖ a positive resistor

Let $R_1 = R_2 = \frac{1}{10}$. We get $R_{in} = \frac{\frac{1}{10} \cdot \frac{1}{10}}{\frac{2}{10} - \frac{5}{10}} = -\frac{1}{30} \Omega$

↖ a negative resistor!

Input power from the source h is

$$P = h^2 R_{in} = h^2 \left(-\frac{1}{30}\right) = -\frac{h^2}{30}$$

↖ a negative number

This means that ^{positive} power is flowing from this

toward the left into the source h :



Question: Where does that power come from?

Answer: From the dependent source.

I will discuss this further.

(Equal to the negative of the power dissipated in the resistors.)