

ESE 271

Final Exam

Name:

Spring, 2003

ID Number:

Do not place your answers on this front page.

Prob. 1 (30 points):


Prob. 2 (25 points):

Prob. 3 (30 points):

Prob. 4 (15 points):

Prob. 1 (30 points):

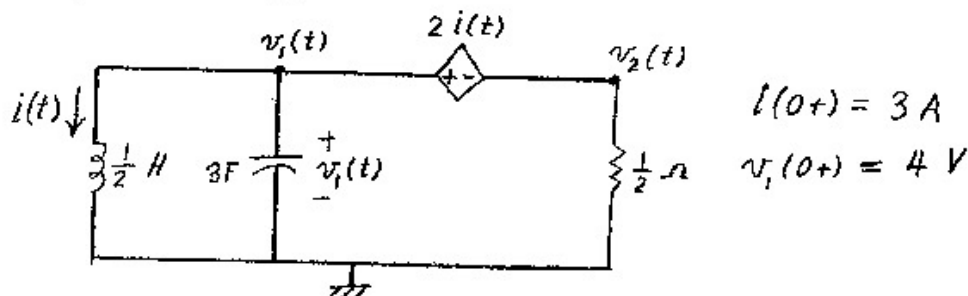Using a nodal analysis, find the Laplace transform $V_1(s)$ of the node voltage $v_1(t)$. Use Cramer's rule and write your answer as a determinant over a determinant. (You may do this either by first writing the integrodifferential equations or first making the transformed network. Write your answer neatly.)



By INTEGRO-DIFFERENTIAL EQUATIONS:

INSIDE BALLOON AROUND THE DEPENDENT SOURCE:

$$v_1 - v_2 = 2i = 2 \left(-\frac{1}{2} \int_0^t v_1(x) dx + 3 \right)$$

$$S_0, \quad v_1 - v_2 = \frac{4}{s} v_1 + \frac{6}{s} \quad \text{OR,} \quad v_1 \left(1 - \frac{4}{s} \right) - v_2 = \frac{6}{s}$$

KCL ON THE OTHER BALLOON:


$$-\frac{1}{2} \int_0^t v_1(x) dx + 3 + 3 \frac{dv_1}{dt} + \frac{v_2}{2} = 0$$

$$S_0, \quad \frac{2}{s} v_1 + \frac{3}{s} + 3(s v_1 - 4) + 2v_2 = 0 \quad \text{OR,} \quad v_1 \left(3s + \frac{2}{s} \right) + 2v_2 = 12 - \frac{3}{s}$$

THUS,

$$V_1 = \frac{\begin{vmatrix} \frac{6}{s} & -1 \\ 12 - \frac{3}{s} & 2 \end{vmatrix}}{\begin{vmatrix} 1 - \frac{4}{s} & -1 \\ 3s + \frac{2}{s} & 2 \end{vmatrix}}$$

USING THE TRANSFORMED CIRCUIT:

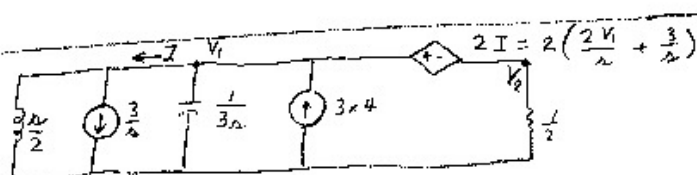

$$\text{INSIDE BALLOON:} \quad v_1 - v_2 = \frac{4}{s} v_1 + \frac{6}{s} \quad \text{OR,} \quad v_1 \left(1 - \frac{4}{s} \right) - v_2 = \frac{6}{s}$$

$$\text{ON BALLOON} \quad \frac{2v_1}{s} + \frac{3}{s} + 3s v_1 - 12 + 2v_2 = 0 \quad \text{OR,} \quad v_1 \left(\frac{2}{s} + 3s \right) + 2v_2 = 12 - \frac{3}{s}$$

ANOTHER CORRECT ANSWER IS GIVEN BY MULTIPLYING THE EQUATIONS BY 4:


$$V_1 = \frac{\begin{vmatrix} 6 & -4 \\ 12 - 3 & 2s \end{vmatrix}}{\begin{vmatrix} 1 - 4 & -1 \\ 3s^2 + 2 & 2s \end{vmatrix}}$$

$$\begin{cases} v_1 (s - 4) - v_2 = 6 \\ v_1 (3s^2 + 2) + 2s v_2 = 12s - 3 \end{cases}$$

Prob. 2 (25 points):

The initial charges on the capacitors are 0. The input voltage is the unit step function $u(t)$.

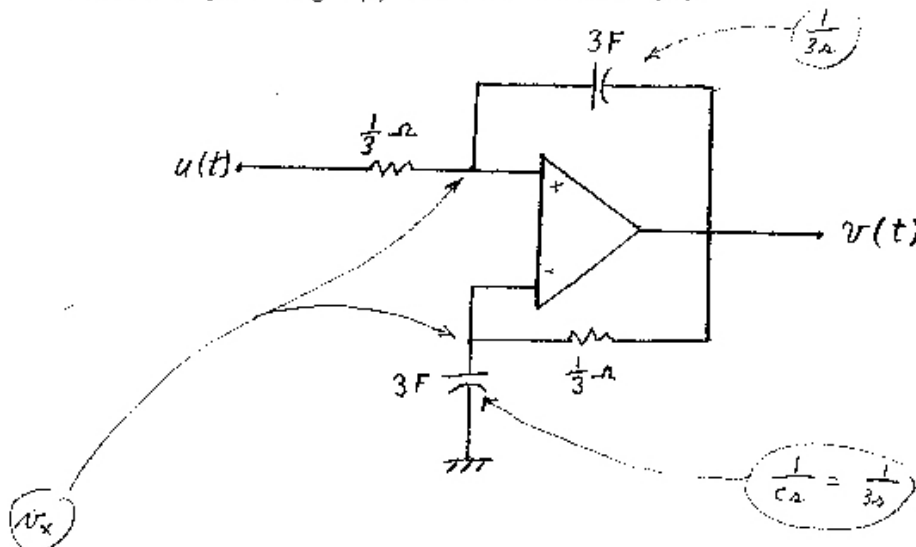Find the output voltage $v(t)$ as a function of time $t > 0$.



AT UPPER NODE FOR V_x :

$$\frac{V_x - \frac{1}{A}}{\frac{1}{3}} + \frac{V_x - V}{\frac{1}{3\Omega}} = 0$$

$$V_x (3 + 3A) - 3AV = \frac{3}{A}$$

AT LOWER NODE FOR V :

$$\frac{V_x}{\frac{1}{3A}} + \frac{V_x - V}{\frac{1}{3}} = 0$$

$$V_x (3 + 3A) - 3V = 0$$

SUBTRACT 2nd EQUATION FROM THE FIRST ONE:

$$3V - 3AV = \frac{3}{A}$$


$$V = \frac{\frac{1}{A}}{1-A} = \frac{-1}{A(A-1)} = \frac{A}{A} + \frac{B}{A-1}$$

$$A = \frac{-1}{-1} = 1, \quad B = -1$$


So, $v(t) = 1 - e^t$ for $t > 0$.

Prob. 3 (30 points):

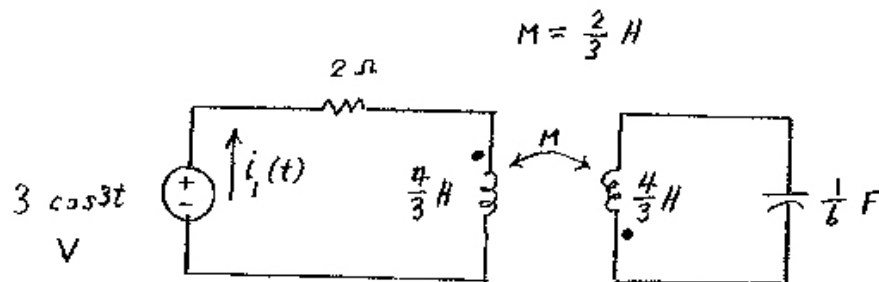This circuit having a nonideal transformer is in the AC steady state. Find the current $i_1(t)$ flowing upward through the source. Write your answer as a cosinusoid.



USE A MESH ANALYSIS WITH MESH CURRENTS

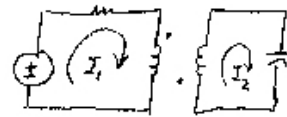

1ST LOOP: $-3 + I_1 (2 + j4) + j2 I_2 = 0$

2ND LOOP: $j4 I_2 + \frac{1}{j3 \times \frac{1}{6}} I_2 + j2 I_1 = 0$

FROM 2ND EQUATION: $I_2 (j4 - j2) + I_1 (j2) = 0$ THUS, $I_2 = -I_1$

FROM 1ST EQUATION: $-3 + I_1 (2 + j4) - j2 I_1 = 0$

$$I_1 = \frac{+3}{2 + j2} = \frac{+3}{2\sqrt{2} \angle 45^\circ} = \frac{3}{2\sqrt{2}} \angle -45^\circ$$

$$i_1(t) = \frac{3}{2\sqrt{2}} \cos(3t + 135^\circ) = 1.06 \cos(3t - 45^\circ)$$

Prob. 4 (15 points):

Find the initial value $f(0+)$ and the initial slope $f'(0+)$ of the function $f(t)$ whose Laplace transform is

$$F(s) = \frac{4s^3 + 3s^2 - 2s + 6}{2s^4 + 6s^3 + 8s^2 + 4s}$$

This $f(t)$ has a final value $f(\infty)$. (Take my word for it.) Find $f(\infty)$.

$$f(0+) = \lim_{s \rightarrow \infty} s F(s) = \lim_{s \rightarrow \infty} \frac{4s^4 + \dots}{2s^4 + \dots} = 2$$

$$\begin{aligned} f'(0+) &= \lim_{s \rightarrow \infty} s (s F(s) - f(0+)) \\ &= \lim_{s \rightarrow \infty} s \left(\frac{4s^4 + 3s^3 - 2s^2 + 6s - 2(2s^4 + 6s^3 + 8s^2 + 4s)}{2s^4 + 6s^3 + 8s^2 + 4s} \right) \\ &= \lim_{s \rightarrow \infty} \frac{-9s^4 + \dots}{2s^4 + \dots} = -4.5 \end{aligned}$$

$$f(\infty) = \lim_{s \rightarrow 0+} s F(s) = \frac{6}{4} = \frac{3}{2}$$