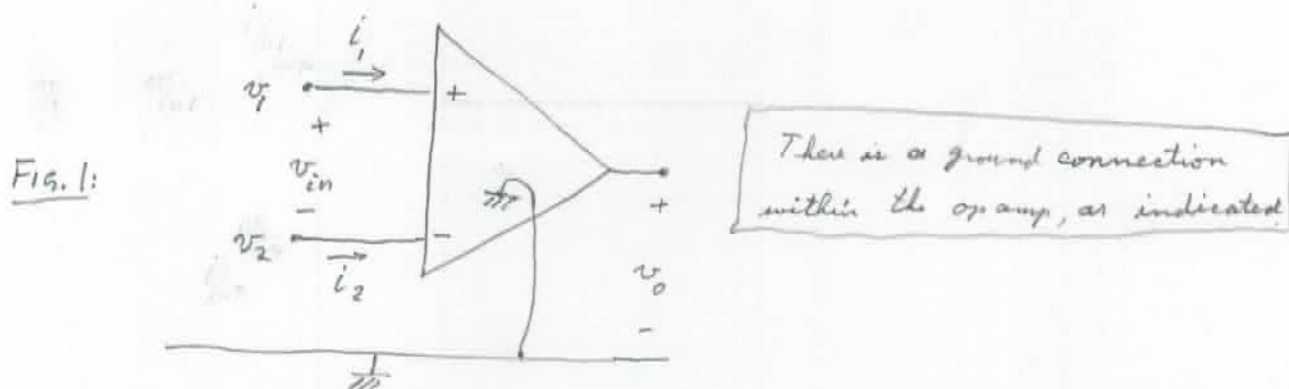


Operational Amplifiers (called OP-AMPS) are specialized amplifiers having extremely high voltage gains (typically, 10^5) and very large input resistance (perhaps $10^6 \Omega$ when the other resistors connected to the op-amp have values in the 10^3 range).


The circuit symbol and its relation to the ground node is:



v_1 and v_2 are node voltages measured with respect to ground.

Thus, $v_{in} = v_1 - v_2$

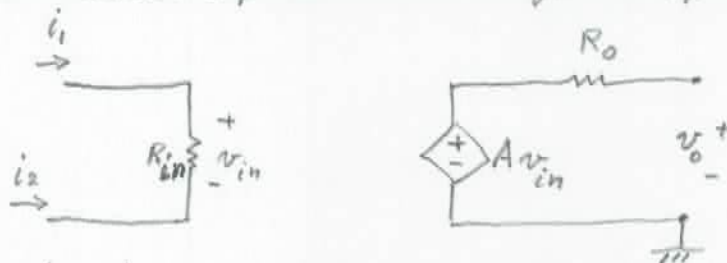Case 1: A quite accurate equivalent circuit for the op-amp is:



Hence, $i_1 = -i_2$

Possible parameter values are:

$R_{in} = 1 M\Omega = 10^6 \Omega$

$R_o = 30 \Omega$

$A = 10^5$

(OR)

$R_{in} = 10^9 \Omega$

$R_o = 300 \Omega$


$A = 10^5$

Case 2: An ideal case arises when we set $R_{in} = \infty$, $R_o = 0$, $A = 10^5$


Case 3: A still more ideal case (called the virtual-short virtual-open model) arises when $v_{in} = 0$ and $i_1 = i_2 = 0$ and v_o is determined by the circuit connected around the op-amp.

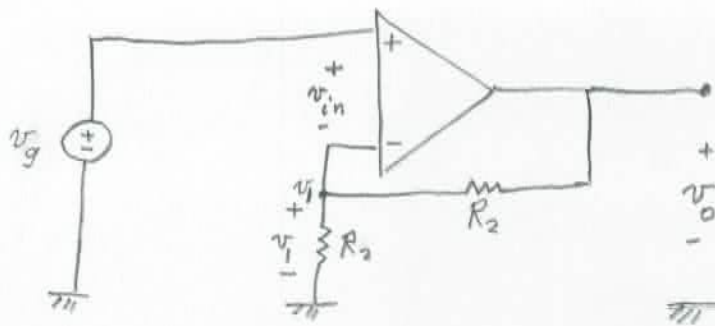Example for Case 1:

Let us first consider a circuit where the op-amp has the equivalent circuit of Case 1:



Upon replacing the op-amp by its equivalent circuit (Case 1), we get

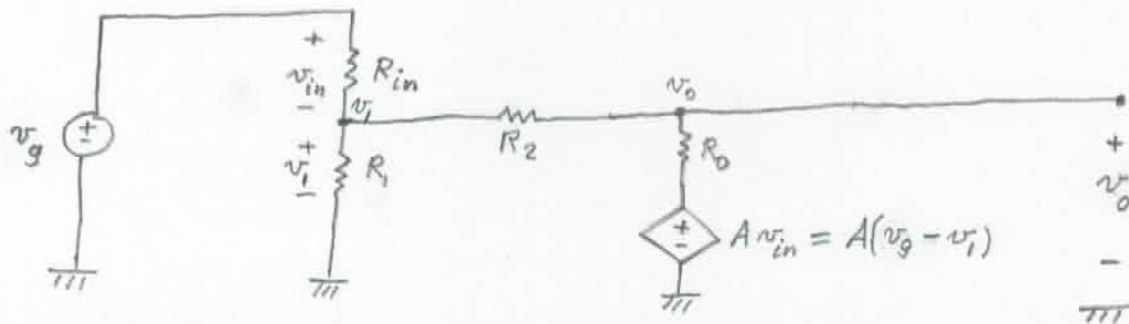

Case 1:

KCL at the v_i node:

$$\textcircled{1} \quad \frac{v_i - v_g}{R_{in}} + \frac{v_i}{R_1} + \frac{v_i - v_o}{R_2} = 0$$

KCL at the v_o node:

$$\textcircled{2} \quad \frac{v_o - v_i}{R_2} + \frac{v_o - A v_g + A v_i}{R_0} = 0$$

v_i and v_o are the only two unknowns in these two equations.

So, we can solve for v_o to get

v_o in terms of v_g and the resistors and A .

Case 2: We will solve for v_o assuming $R_{in} = \infty$ and $R_0 = 0$

(actually, R_{in} is very big and R_0 is very small compared to other resistors.)

$$\text{From } \textcircled{1}: 0 + v_i \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_o}{R_2}. \quad \text{Thus, } v_o = v_i \left(1 + \frac{R_2}{R_1} \right) \quad \leftarrow \textcircled{3}$$

From $\textcircled{2}$: Since $\frac{1}{R_0}$ is much bigger than $\frac{1}{R_2}$, we can neglect $\frac{v_o - v_i}{R_2}$ in $\textcircled{2}$.

$$\text{Thus, } v_o = A(v_g - v_i). \quad \text{So, } v_i = v_g - \frac{v_o}{A} \quad \leftarrow \textcircled{4}$$

Now, put $\textcircled{4}$ into $\textcircled{3}$: We get $v_o = \left(v_g - \frac{v_o}{A} \right) \left(1 + \frac{R_2}{R_1} \right)$

Solve for v_o . See next page.

$$\text{So, } v_o = v_g \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 + \frac{1 + \frac{R_2}{R_1}}{A}}$$

This is v_o
in Case 2. (The ideal op amp.)

Case 3: The virtual-short virtual open case: $A = \infty$.


$$\textcircled{5} \quad \text{So, } v_o = v_g \left(1 + \frac{R_2}{R_1}\right)$$

This same result occurs when we take $i_1 = i_2 = v_{in} = 0$ in Fig. 1 (on page OP AMP 1).

$v_{in} = 0$ is the "virtual short" condition.

$i_1 = i_2$ is the "virtual" open condition

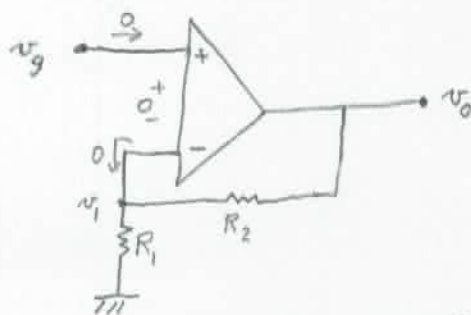We can get $\textcircled{5}$ directly as follows:



So by virtual-short condition, $v_1 = v_g$.


By virtual-open condition, R_1 and R_2 are effectively in series.

So, by the voltage-divider rule,

$$v_g = v_1 = v_o \frac{R_1}{R_1 + R_2}. \quad \text{Therefore, } v_o = v_g \left(1 + \frac{R_2}{R_1}\right). \quad \text{done.}$$

The voltage follower: Also called the unity gain amplifier:

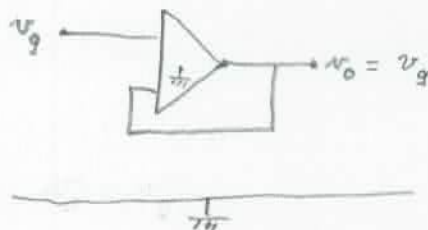This occurs in Case 3 when we set $R_1 = \infty$ and $R_2 = 0$.




We will now analyze some more input-output equations

OP AMP 4

(i.e., "transfer functions")

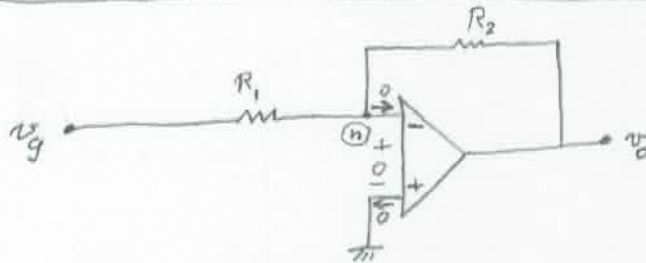for other circuits containing the virtual-short virtual-open model of the OP AMP.



Note: The "feedback" is to the negative terminal of the OP AMP


At node (n), the node voltage is 0.

So, by KCL at (n):
$$\frac{v_g - 0}{R_1} + \frac{v_o - 0}{R_2} + 0 = 0$$
 (current into OP AMP = 0)


So
$$v_o = - \frac{R_2}{R_1} v_g$$
 (The "transfer function" is
$$\frac{v_o}{v_g} = - \frac{R_2}{R_1}$$
)

This is called an "INVERTER"

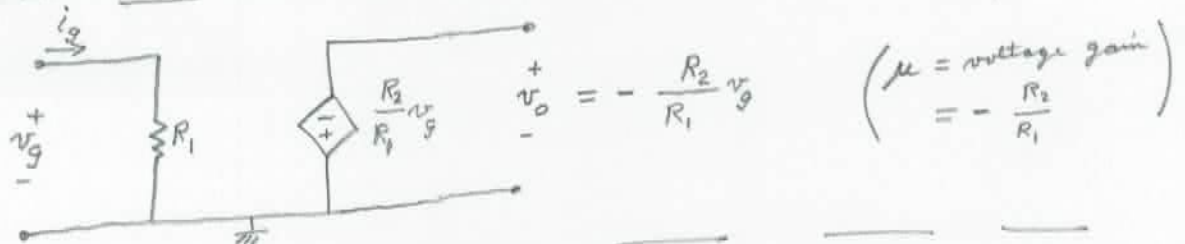
It is a VCVS and has the equivalent circuit:



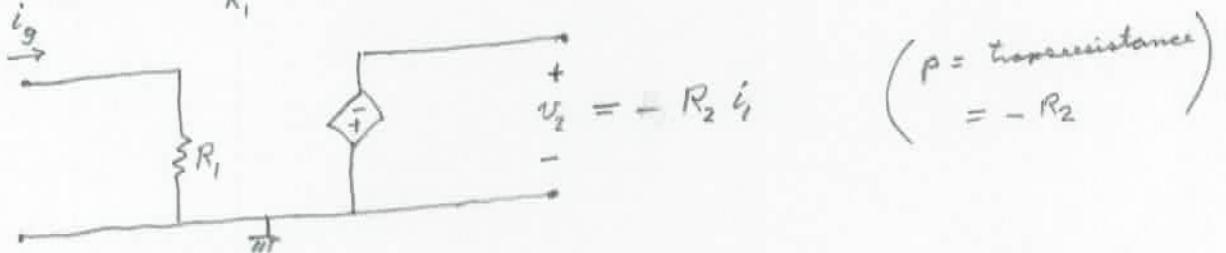If we use $i_g = \frac{v_g}{R_1}$ as the input variable, we get a VCCS:




Here is a special way of getting a CCCS:

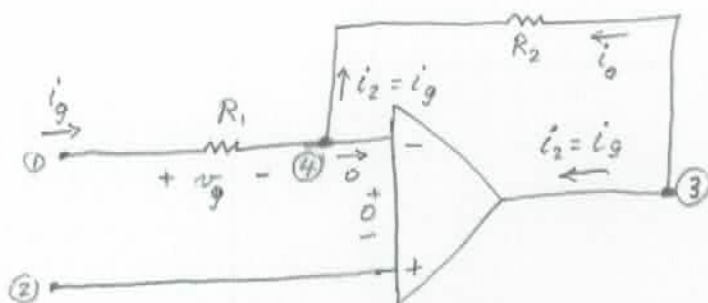

$$i_2 = i_g = \frac{v_g}{R_1}$$


The equivalent circuit is:

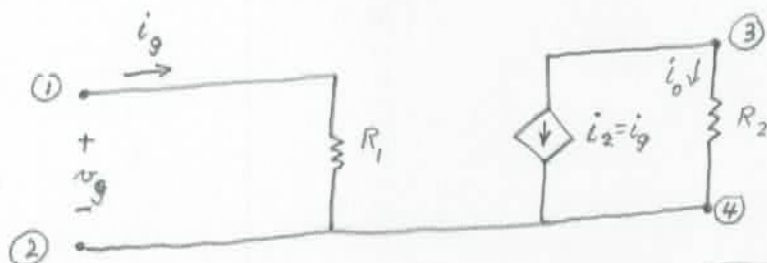

$$i_o = -i_2 = -i_g$$


$$\left(\begin{array}{l} \beta = \text{current gain} \\ = -1 \end{array} \right)$$

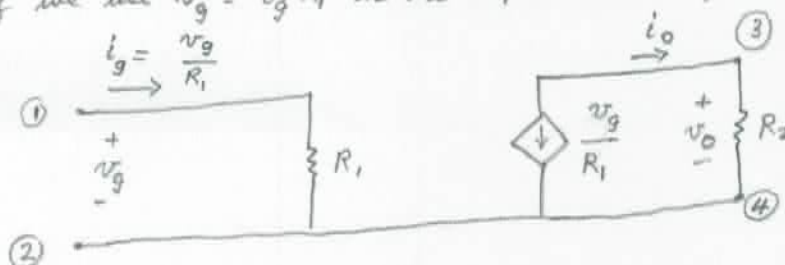If we use $v_g = i_g R_1$ as the input variable, we get a VCCS:



$$i_o = -\frac{v_g}{R_1}$$

$$\left(\begin{array}{l} g = \text{transconductance} \\ = -\frac{1}{R_1} \end{array} \right)$$

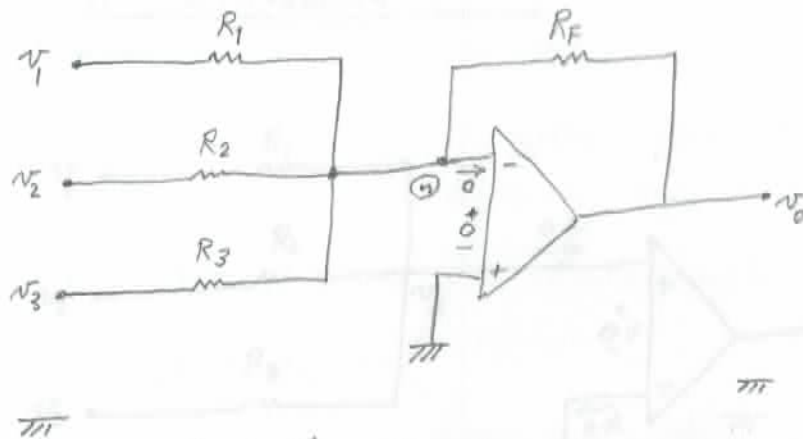AN INVERTING SUMMER

Again, the node voltage at ① is 0.

By KCL at node ①:

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} + \frac{v_0}{R_F} = 0$$

$$\text{So, } v_0 = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 - \frac{R_F}{R_3} v_3$$

If we choose $R_F = R_1 = R_2 = R_3$, we get

$$v_0 = -v_1 - v_2 - v_3$$

Also, by the voltage divider equation at the load v_L node:

$$v_L = \frac{R_L}{R_L + R_4} v_0 \Rightarrow v_0 = \left(1 + \frac{R_4}{R_L}\right) v_L$$

So, putting these equations together, we get

$$v_0 = \left(1 + \frac{R_4}{R_L}\right) \left(-\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 - \frac{R_F}{R_3} v_3 \right)$$

A special case, when the non-inverting input is grounded and $R_4 = 0$.

Then the equation is that:

$$\left(1 + \frac{R_4}{R_L}\right) \frac{R_F}{R_1} = 1, \quad \left(1 + \frac{R_4}{R_L}\right) \frac{R_F}{R_2} = 1, \quad \left(1 + \frac{R_4}{R_L}\right) \frac{R_F}{R_3} = 1$$

(Note that $\frac{R_F}{R_L} \ll 1$ for $k \gg 1$)

$$\text{Then, } v_0 = -v_1 - v_2 - v_3$$

$$R_F = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

The parallel
resistors
for R_1, R_2, R_3