

Energy Storage Elements

A little later on, we will be talking about AC (alternating current) circuits.

In that case, two new kinds of elements arise:


Capacitors and Inductors.

These elements store energy, but do not dissipate them as do resistors.


So, let's talk about them first.

Capacitors, C:

Symbol:

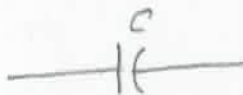

Basic formula:

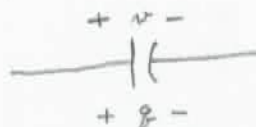

"electrical charge"

→ "charge"

$q = C v$

"voltage"

C = a constant, called "capacitance" or "capacitor"

Units: Coulombs

farads



volts

The straight and curved lines are not significant. We can also write

+ v -
+ q -

$q = q(t)$ and $v = v(t)$ can vary with time.

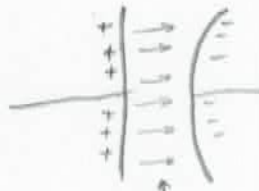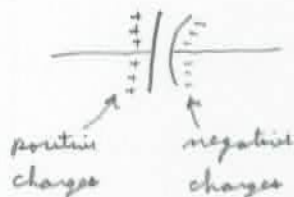$i(t) = \frac{dq(t)}{dt}$ is the current. It equals the rate of change of q .



The "electric field" inside the capacitor stores electrical energy.

Energy storage in a capacitor.

C-L-2

Assuming $v(x)$ and $i(x)$ are both 0 for all sufficiently small x , the energy $w_c(t)$ stored in C at time t is

$$w_c(t) = \int_{-\infty}^t \underbrace{v(x) i(x)}_{\substack{\uparrow \\ \text{"power" going into } C}} dx$$

$$\begin{array}{c} i(x) + q(x) - \\ \hline + v(x) - \\ i(x) = \frac{dq(x)}{dx} \end{array}$$

$$w_c(t) = \int_{-\infty}^t v(x) C \frac{dv(x)}{dx} dx$$

$$= C \int_0^{v(t)} v dv$$

← Change of variable for the integration.


$$= C \frac{v^2}{2} \text{ joules}$$

(Joules is the units for energy)

$$= \frac{q^2}{2C} \text{ joules}$$

$$\leftarrow \text{But } q = Cv, \quad v = \frac{q}{C}$$

Example: Assume

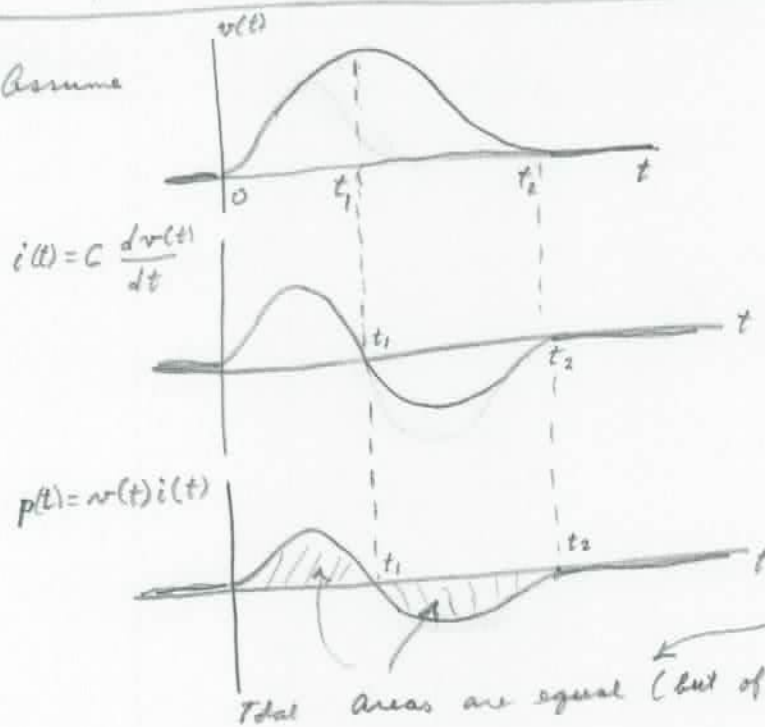

On the "upswing" between 0 and t_1 , the capacitor is "charging up" - its energy storage is increasing.

On the "downswing" between t_1 and t_2 , the capacitor is "discharging" - its energy storage is decreasing.

At and after t_2 , as much energy is returned to the electrical source via discharge as the capacitor received from the electrical source during the charging phase.

The basic differential equation for a capacitor C is

$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt}(Cv(t)). \quad \text{That is, } i(t) = C \frac{dv(t)}{dt}$$

amperes farads volts
seconds

Again: $i(t) = C \frac{dv(t)}{dt}$

$$\boxed{\text{amperes} = \frac{\text{farads} \times \text{volts}}{\text{seconds}}}$$


This simple differential equation can be solved to get $v(t)$ in terms of $i(t)$ if we know an initial value $v(t_0)$.

$$v(t) = \frac{1}{C} \int_{t_0}^t i(x) dx + v(t_0)$$

If $v(t_0) = 0$ at t_0 , we get $v(t) = \frac{1}{C} \int_{t_0}^t i(x) dx$.

Or, if $v(t) \rightarrow 0$ as $t \rightarrow -\infty$, we get $v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx$.

Capacitors in "parallel":

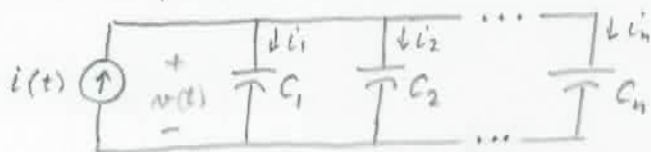

$$\begin{aligned} \text{KCL: } i(t) &= i_1(t) + i_2(t) + \dots + i_n(t) = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt} \\ &= (C_1 + C_2 + \dots + C_n) \frac{dv}{dt} \end{aligned}$$


Effectively, we have an equivalent capacitor C_p for the parallel capacitors

$$= C_p \frac{dv}{dt}$$

$$i(t) \text{ in parallel with } C_p = C_1 + C_2 + \dots + C_n, \quad i(t) = C_p \frac{dv}{dt}$$

In words, capacitors in parallel add up.

Capacitors in series:

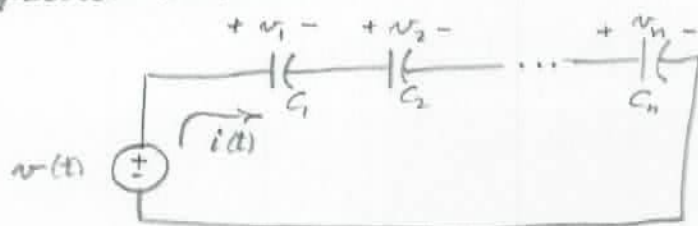

$$v(t) = v_1(t) + v_2(t) + \dots + v_n(t)$$


$$= \frac{1}{C_1} \int_{t_0}^t i(x) dx + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(x) dx + v_2(t_0) + \dots + \frac{1}{C_n} \int_{t_0}^t i(x) dx + v_n(t_0)$$

$$\text{But } v(t_0) = v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)$$

So effectively we have an equivalent series capacitor C_S :

$$v(t) = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right) \int_{t_0}^t i(x) dx + v(t_0)$$


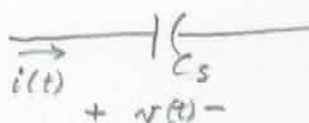
$$= \frac{1}{C_S} \int_{t_0}^t i(x) dx + v(t_0)$$



$$C_S = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

That is, capacitors in series combine according to this formula.

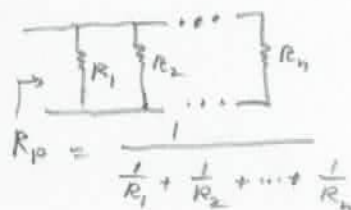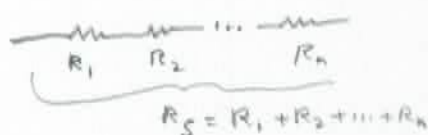
(Note: This is just the reverse of how resistors combine in series and in parallel.)



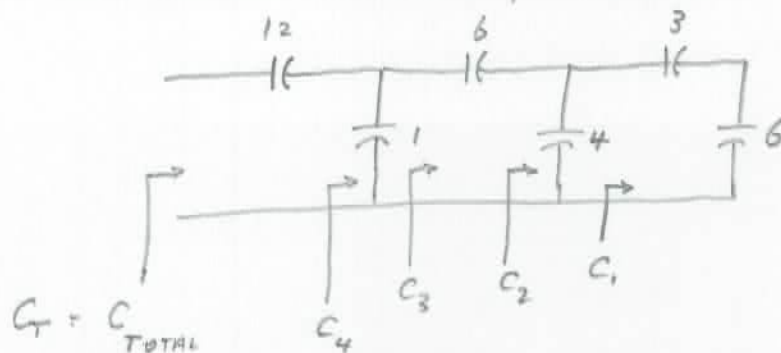Example:

C-2-5

A series-parallel connection of capacitors:



All capacitor units
are μF
microfarads
 $= 10^{-6}$ farads.

(A more common
capacitance value.)

$$C_1 = \frac{1}{\frac{1}{3} + \frac{1}{6}} = \frac{3 \times 6}{3 + 6} = 2 \mu F$$

$$C_2 = 4 + 2 = 6$$

$$C_3 = \frac{1}{\frac{1}{6} + \frac{1}{6}} = 3$$

$$C_4 = 1 + 3 = 4$$


$$C_T = \frac{1}{\frac{1}{12} + \frac{1}{4}} = \frac{12 \times 4}{12 + 4} = 3 \mu F$$

Inductances combine the way resistors combine!



← Inductors in series
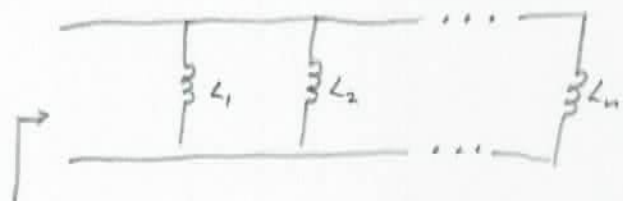
$$\text{Total series inductance} = L_s = L_1 + L_2 + \dots + L_n$$






← Inductors in parallel

$$\text{Total parallel inductance} = L_p = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}}$$

Cosinusoidal signals

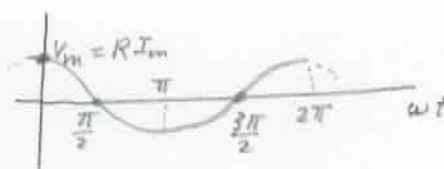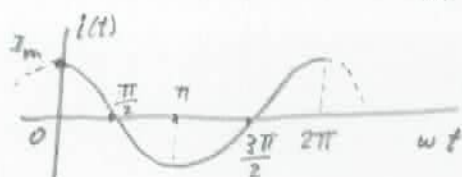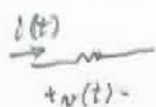For a resistor R : $v(t) = R i(t)$ or $V_m \cos \omega t = R I_m \cos \omega t$



Let f = frequency = number of cycles per second (cps)





$\omega = 2\pi f$ = number of radians per second (rad./sec)

(For power works, $f = 60$ cps. So $\omega = 2\pi \times 60 = 120\pi$ rad./sec. ≈ 377 rad./sec.)

For a capacitor: $i(t) = C \frac{dv}{dt}$

So, when $v(t) = V_m \cos \omega t$, we have $i(t) = C V_m (-\omega \sin \omega t)$
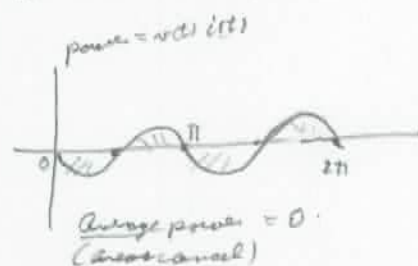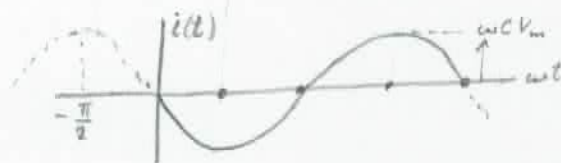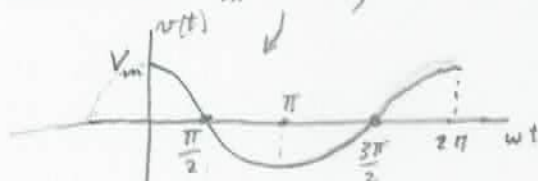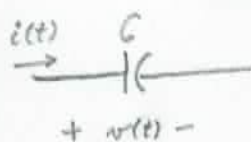
$$= \omega C V_m \cos(\omega t + 90^\circ)$$





So the current "peaks" at $\frac{\pi}{2}$ radians before the voltage "peaks".

We say that, in a capacitor, "the current leads the voltage by $90^\circ (= \frac{\pi}{2})$ "
(or that "the voltage lags the current by 90° ".)


For an inductor: $v(t) = L \frac{di}{dt}$

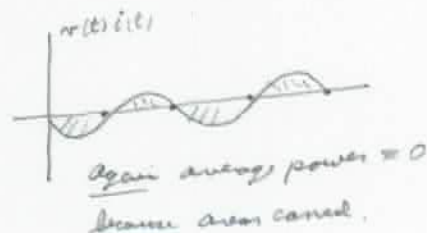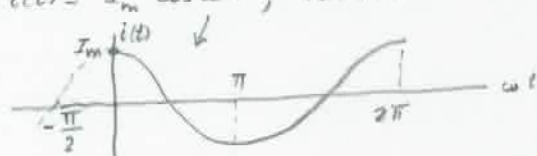When $i(t) = I_m \cos \omega t$, we have $v(t) = \omega L I_m \cos(\omega t + 90^\circ)$



So now the voltage peaks at $\frac{\pi}{2}$ radians before the current peaks.

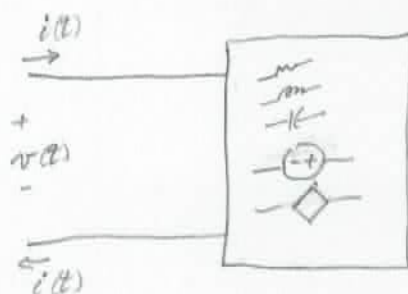We say that in a inductor, "the current lags the voltage by 90° "
(or that "the voltage leads the current by 90° ".)



For a general network, we conventionally talk about the current "lagging" or "leading" the voltage by the phase angle θ . Also called the "power factor angle"


and we write

$$v(t) = V_m \cos(\omega t + \phi_v)$$

$$i(t) = I_m \cos(\omega t + \phi_i) \quad , \text{ where } \phi_v - \phi_i = \theta$$

More simply, if $v(t) = V_m \cos \omega t$, we have $i(t) = I_m \cos(\omega t - \theta)$.

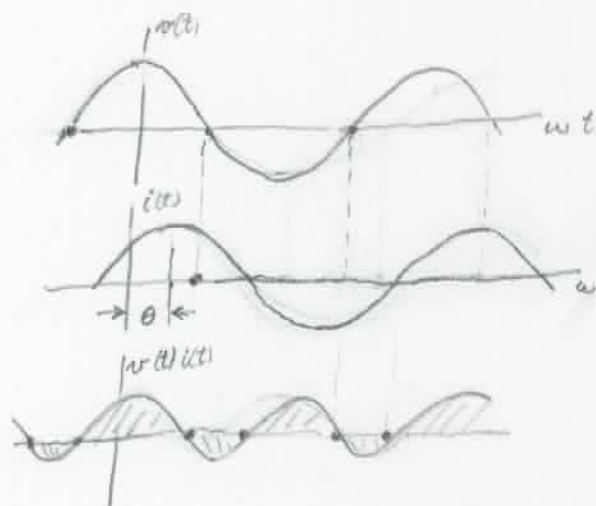So the power-factor angle is taken to be positive when $v(t)$ leads $i(t)$ by θ and is taken to be negative when $v(t)$ lags $i(t)$ by θ .



Curve drawn with $0 < \theta < 90^\circ$

In this case, areas do not cancel and we have

P_{av} = average power

$$P_{av} = \frac{V_m I_m}{2} \cos \theta$$

We will derive this later on.

This is conventionally done.

If we use effective values for $v(t)$ and $i(t)$: $V_{eff} = \frac{V_m}{\sqrt{2}}$, $I_{eff} = \frac{I_m}{\sqrt{2}}$, the formula simplifies to $P_{av} = V_{eff} I_{eff} \cos \theta$.