

ESE 271
Fall, 2008

Second Exam

Name:
ID Number:

Do not place your answers on this front page.
Each problem is worth 25 points.

Prob. 1:

Prob. 2:

Prob. 3:

Prob. 4:

Prob. 1:

Find the single cosinusoid $A_m \cos(3t + \phi)$ that is equal to

$$5 \cos(3t + 30^\circ) - 8 \sin(3t + 135^\circ)$$

That is, determine A_m and ϕ .

(You may work to four significant figures with your numbers.)

$$5 \cos(3t + 30^\circ) + 8 \cos(3t + 135^\circ + 90^\circ)$$

↓

$$5 \angle 30^\circ + 8 \angle 225^\circ$$

$$= 5 \cos 30^\circ + j 5 \sin 30^\circ + 8 \cos 225^\circ + j 8 \sin 225^\circ$$

$$= 4.330 + j 2.500 - 5.657 - j 5.657$$

$$= -1.327 - j 3.157$$

$$= 3.425 \angle 247.2^\circ = 3.425 \angle -112.8^\circ$$



Thus,

$$A_m = 3.42$$

$$\phi = 247.2^\circ \quad \text{OR} \quad \phi = -112.8^\circ$$

Prob. 2:

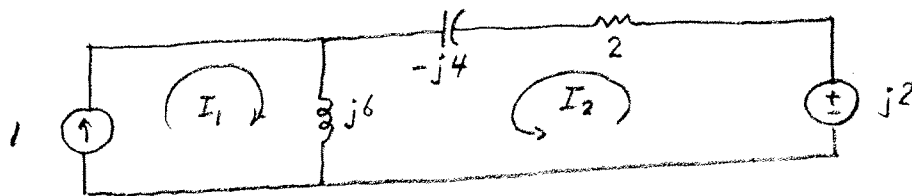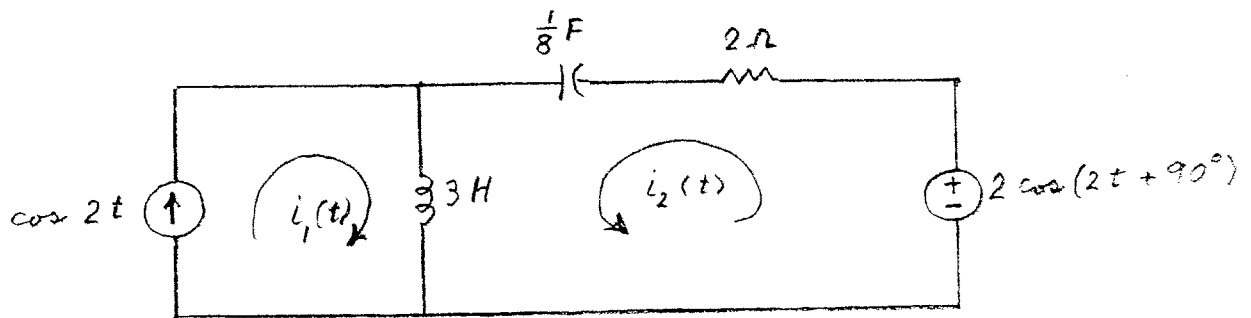Do a mesh analysis using the mesh currents shown to determine $i_2(t)$ as a cosinusoid.



$$I_1 = 1$$

KVL AROUND I_2 MESH:

$$-j2 + (2 - j4)I_2 + (I_1 + I_2)j6 = 0$$


$$I_2 = \frac{-j2}{1+j} = \sqrt{2} \angle -135^\circ$$

So,

$$i_2(t) = \sqrt{2} \cos(2t - 135^\circ)$$


Prob. 3:

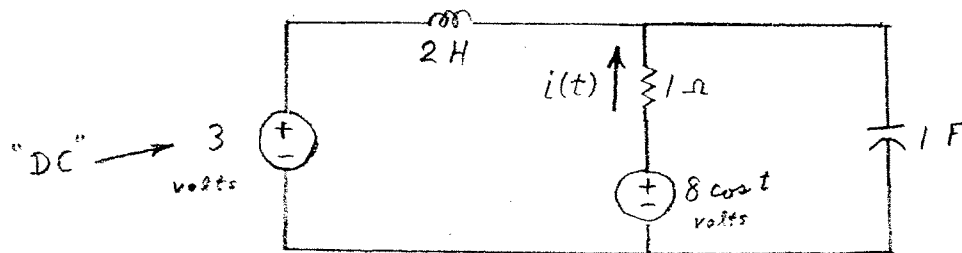Find the effective value of the current $i(t)$ in the $1\ \Omega$ resistor.




By SUPERPOSITION:

FOR THE 3 V SOURCE ALONE:

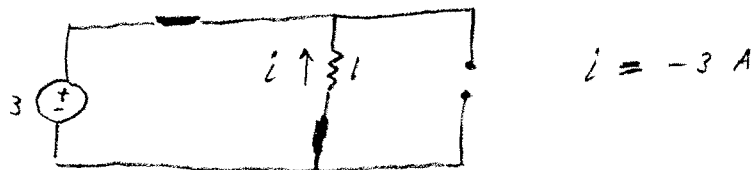

FOR THE $8 \cos t$ SOURCE ALONE

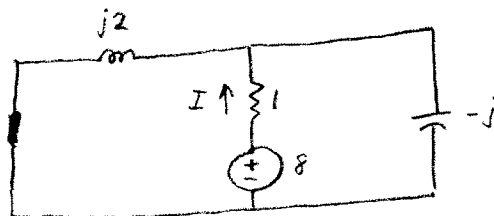

$$I = \frac{8}{1 + \frac{(j2)(-j)}{j2 - j}} = \frac{8}{1 - j2} = \frac{8}{\sqrt{5}} \angle \theta$$



$$\left(\theta = -\tan^{-1} \frac{-2}{1} \right)$$

(WE DO NOT NEED θ)

$$I_{\text{eff}} = \sqrt{(-3)^2 + \frac{(8/\sqrt{5})^2}{2}} = 3.924\text{ A}$$

Prob. 4:

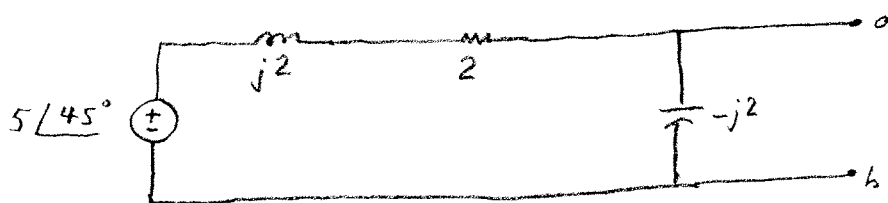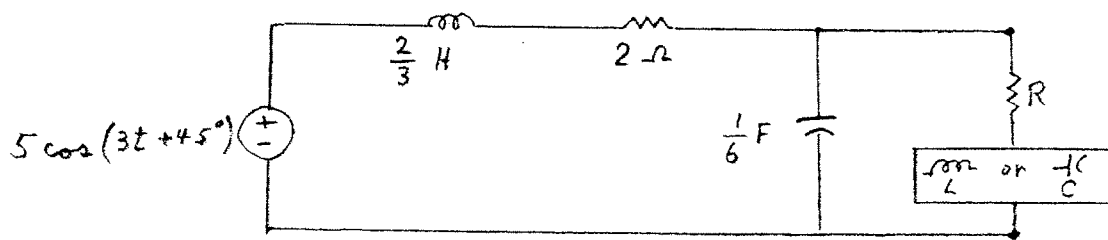- (a) Find R and either L or C to maximize the dissipated power P in R .
 (b) What is that maximum power P_{max} ?




As seen from terminals a and b:

$$V_{oc} = 5 \angle 45^\circ \frac{-j2}{j2 + 2 - j2} = 5 \angle -45^\circ$$

$$Z_{TH} = \frac{(-j2)(2 + j2)}{-j2 + 2 + j2} = 2 - j2$$

So,

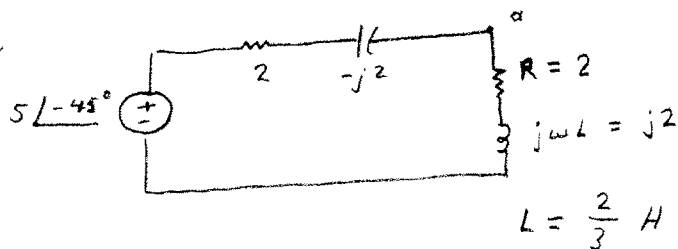

WE MUST HAVE
AN INDUCTOR HERE
IN ORDER TO MAXIMIZE.

Finally,

$$P_{max} = \frac{|V_{oc}|^2}{4R} = \frac{25}{8} \text{ W} = 3.125 \text{ W}$$