

ESE 271

Final Exam

Name:

Spring, 2002

ID Number:

Do not place your answers on this front page.

Prob. 1 (15 points):

Prob. 2 (25 points):

Prob. 3 (30 points):


Prob. 4 (30 points):

Prob. 1. (15 points):


(a) Find the Laplace transform of the single triangular pulse:



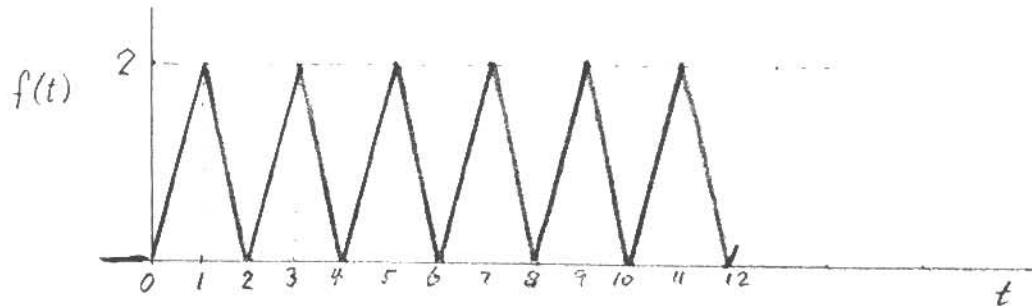(b) Find the Laplace transform of the pulse train, which continues infinitely to the right.



(a) To first get the transform of

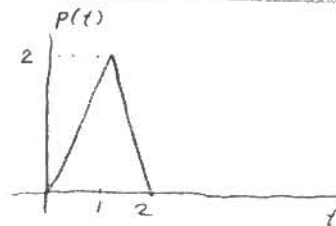

$$p(t) = 2t u(t) - 4(t-1)u(t-1) + 2(t-2)u(t-2)$$

$$P(s) = \frac{2}{s^2} - \frac{4}{s^2} e^{-s} + \frac{2}{s^2} e^{-2s}$$


(b) Then,

$$F(s) = P(s) (1 + e^{-2s} + e^{-4s} + e^{-6s} + \dots)$$

$$= \frac{P(s)}{1 - e^{-2s}}$$


**Prob. 2:** (25 points):

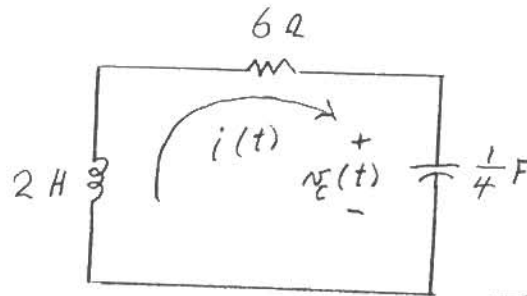Find the time function  $i(t)$  by using the Laplace-transformed circuit with the initial-condition sources in Thevenin form.



$$i(0+) = 3 \text{ A}$$

$$v_c(0+) = 4 \text{ V}$$

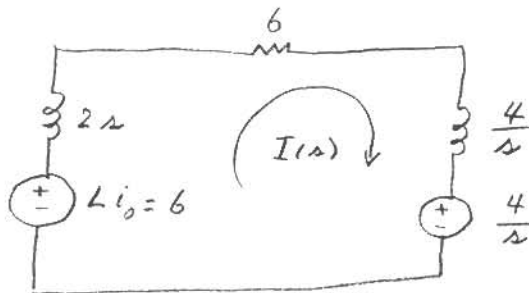

$$I(s) = \frac{6 - \frac{4}{s}}{2s + 6 + \frac{4}{s}} = \frac{6s - 4}{2s^2 + 6s + 4} = \frac{6s - 4}{2(s+1)(s+2)}$$

$$\left. \begin{matrix} p_1 \\ p_2 \end{matrix} \right\} = \frac{-6 \pm \sqrt{36 - 32}}{4} = \frac{-6 \pm 2}{4} = -1, -2 \quad \curvearrowright$$

$$I(s) = \frac{A}{s+1} + \frac{B}{s+2}$$

$$A = \frac{-6 - 4}{2 \times 1} = -5$$

$$B = \frac{-12 - 4}{2(-1)} = 8$$

$$i(t) = -5e^{-t} + 8e^{-2t} \quad \text{For } t > 0.$$

Prob. 3: (30 points):

Let  $F(s)$  be the Laplace transform of  $f(t)$ , where

$$F(s) = \frac{18s^3 + 1}{(3s^2 + 3)^2}$$

(a) Find  $f(0+)$ .

(b) Find  $f^{(1)}(0+)$ . ( $f^{(1)}$  denotes the first derivative of  $f(t)$ .)

(c) Determine  $f(\infty)$  as a single number, if possible. If not possible, state why it is not possible.

$$(a) \quad F(s) = \frac{18s^3 + 1}{9(s^2 + 1)^2} = \frac{18s^3 + 1}{9(s^4 + 2s^2 + 1)}$$

$$f(0+) = \lim_{s \rightarrow \infty} s F(s) = \lim_{s \rightarrow \infty} \frac{18s^4 + s}{9(s^4 + 2s^2 + 1)} = 2$$

$$(b) \quad f^{(1)}(0+) = \lim_{s \rightarrow \infty} s (s F(s) - f(0+))$$

$$= \lim_{s \rightarrow \infty} s \left( \frac{18s^4 + s}{9s^4 + 18s^2 + 9} - 2 \right)$$

$$= \lim_{s \rightarrow \infty} s \left( \frac{18s^4 + s - 18s^4 - 36s^2 - 18}{9s^4 + 18s^2 + 9} \right)$$



$$= 0$$

(c) ROOTS OF DENOMINATOR ARE AT  $s = \pm j$  (THEY ARE DOUBLE ROOTS)

THUS, THE FINAL-VALUE THEOREM DOES NOT HOLD.

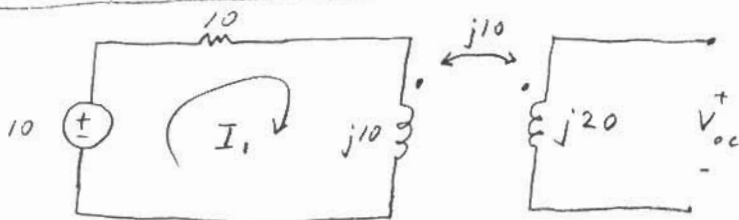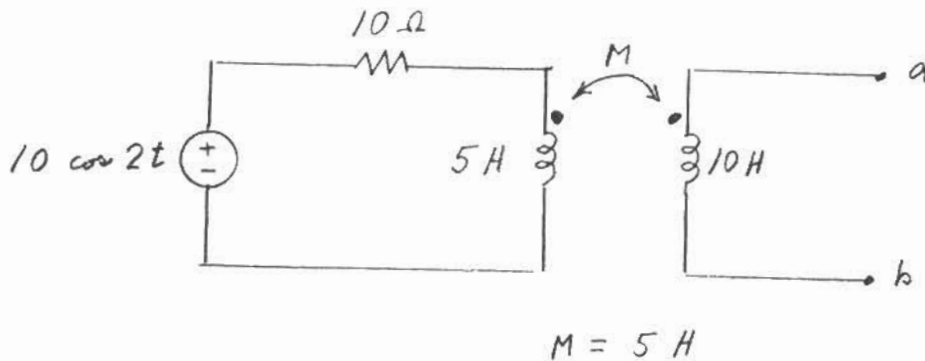**Prob. 4: (30 points):**

Using AC steady state analysis, draw Thevenin's equivalent circuit as seen from the terminals  $a$  and  $b$ . Determine Thevenin's impedance  $Z_{TH}$  and open-circuit voltage  $V_{oc}$  between terminals  $a$  and  $b$  as complex numbers in polar form.




To GET  $V_{oc}$ :

$$I_1 = \frac{10}{10 + j10} = \frac{1}{1 + j} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_{oc} = j10 I_1 = \frac{10}{\sqrt{2}} \angle 45^\circ = 7.071 \angle 45^\circ$$

To GET  $I_{sc}$ :

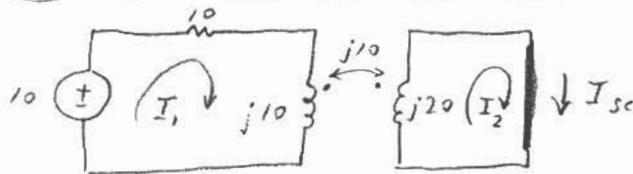

1<sup>st</sup> Loop

$$I_1(10 + j10) - j10 I_2 = 10$$

2<sup>nd</sup> Loop

$$-j10 I_1 + j20 I_2 = 0 \Rightarrow I_1 = 2 I_2$$

$$\text{So, } 2I_2(10 + j10) - j10 I_2 = 10$$

$$I_2 = \frac{10}{20 + j10} = \frac{1}{2 + j} = \frac{1}{\sqrt{5}} \angle -26.57^\circ = 0.4472 \angle -26.57^\circ = I_{sc}$$

$$\text{Thus, } Z_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{7.071 \angle 45^\circ}{0.4472 \angle -26.57^\circ} = 15.81 \angle 71.57^\circ$$



← THEVENIN'S CIRCUIT