

ESE 271  
Fall, 2008

Third Exam

Name:  
ID Number:

Do not place your answers on this front page.  
Each problem is worth 25 points.

Prob. 1:

Prob. 2:

Prob. 3:

Prob. 4:

Prob. 1:

Given that  $f(t) = \cos 3t$  for  $t > 0$ , Find the Laplace transform of

$$\frac{d}{dt} t f(t)$$

You may leave your answer in factored form.

---

$$F(s) = \mathcal{L} f(t) = \frac{s}{s^2 + 3^2}$$

$$\mathcal{L} t f(t) = -\frac{d}{ds} \left( \frac{s}{s^2 + 9} \right) = \frac{s^2 - 9}{(s^2 + 9)^2}$$

$$\mathcal{L} \frac{d}{dt} t f(t) = s \left( \frac{s^2 - 9}{(s^2 + 9)^2} \right) - 0 = \frac{s(s^2 - 9)}{(s^2 + 9)^2}$$

---

ANOTHER WAY:

$$\frac{d}{dt} t \cos 3t = \cos 3t - 3t \sin 3t$$

$$\mathcal{L} \frac{d}{dt} t \cos 3t = \frac{s}{s^2 + 9} - 3 \left( -\frac{d}{ds} \right) \frac{3}{s^2 + 9}$$

$$= \frac{s}{s^2 + 9} + 9 \frac{(-2s)}{(s^2 + 9)^2}$$


$$= \frac{s(s^2 - 9)}{(s^2 + 9)^2}$$

**Prob. 2:**


In the following circuit, the input voltage is

$$v_{in}(t) = u(t) - u(t-2)$$

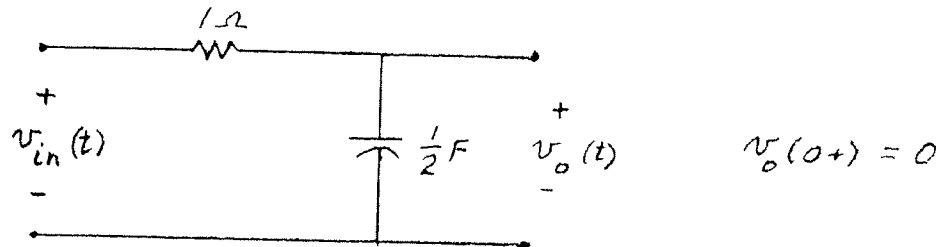Find the output voltage  $v_o(t)$  for  $t > 0$ .



THE TRANSFORMED CIRCUIT IS:

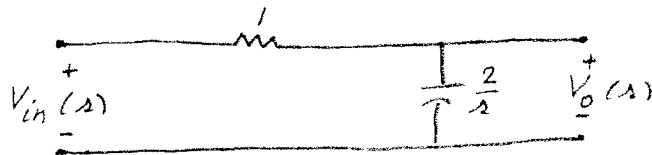

$$V_{in}(s) = \frac{1 - e^{-2s}}{s}$$

$$V_o(s) = V_{in}(s) \cdot \frac{\frac{2}{s}}{1 + \frac{2}{s}}$$

$$V_o(s) = \frac{2}{s+2} \cdot \frac{1 - e^{-2s}}{s} = \left( \frac{A}{s} + \frac{B}{s+2} \right) (1 - e^{-2s})$$

$$A = 1, \quad B = -1$$

So,

$$v_o(t) = 1 - e^{-2t} - u(t-2) + e^{-2(t-2)} u(t-2)$$


WHERE  $t > 0$

OR

$$v_o(t) = u(t) - e^{-2t} u(t) - u(t-2) + e^{-2(t-2)} u(t-2)$$

Prob. 3:

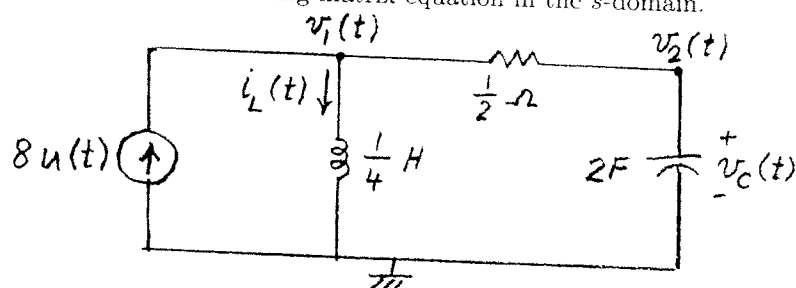At  $t = 0+$ , the initial current  $i_L(0+)$  and initial voltage  $v_C(0+)$  are as shown. Using a nodal analysis for  $t > 0$ , find two equations involving  $V_1(s) = \mathcal{L}\{v_1(t)\}$  and  $V_2(s) = \mathcal{L}\{v_2(t)\}$ , and then fill in the following matrix equation in the  $s$ -domain.



$$i_L(0+) = 5 \text{ A}$$

$$v_C(0+) = v_2(0+) = 3 \text{ V}$$

THE INTEGRODIFFERENTIAL EQUATIONS:

AT  $v_1(t)$  NODE:

$$-8u(t) + \frac{1}{\frac{1}{4}} \int_0^t v_1(x) dx + 5 + \frac{v_1(t) - v_2(t)}{\frac{1}{2}} = 0$$

AT  $v_2(t)$  NODE:

$$\frac{v_2(t) - v_1(t)}{\frac{1}{2}} + 2 \frac{dv_2(t)}{dt} = 0$$

APPLY  $\mathcal{L}$  AND REARRANGE EQUATIONS:

$$\frac{4}{s} V_1(s) + 2 V_1(s) - 2 V_2(s) = \frac{8}{s} - \frac{5}{s} = \frac{3}{s}$$

$$2 V_2(s) - 2 V_1(s) + 2(s V_2(s) - 3) = 0$$

$$\begin{bmatrix} \frac{4}{s} + 2 & -2 \\ -2 & 2s + 2 \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} \frac{3}{s} \\ 6 \end{bmatrix}$$

(WE CAN MULTIPLY THE FIRST EQUATION BY  $s$  (OR ANOTHER FUNCTION OF  $s$ ) TO GET ANOTHER CORRECT ANSWER.)

Prob. 4:

Determine the inverse Laplace transform  $f(t) = \mathcal{L}^{-1}F(s)$  for  $t > 0$ , where

$$F(s) = \frac{s+2}{s^3 + 4s^2 + 5s}$$

$$F(s) = \frac{s+2}{s(s-p_1)(s-p_2)} = \frac{s+2}{s(s^2+4s+5)}$$

$$\left. \begin{matrix} p_1 \\ p_2 \end{matrix} \right\} = \frac{-4 \pm \sqrt{4^2 - 4 \times 5}}{2} = -2 \pm j$$

So,

$$F(s) = \frac{A}{s} + \frac{B}{s+2-j} + \frac{B^*}{s+2+j}$$

$$A = \frac{2}{5}$$

$$B = \frac{-2+j+2}{(-2+j)(-2+j+2+j)} = \frac{1}{2(-2+j)} = \frac{1}{2\sqrt{5} \angle \tan^{-1} \frac{1}{-2}}$$

$$B = \frac{1}{2\sqrt{5}} \angle -153.43^\circ = \frac{1}{2\sqrt{5}} \angle 206.57^\circ$$

So, for  $t > 0$ :

$$f(t) = \frac{2}{5} + 2|B|e^{-\alpha t} \cos(\beta t + \theta)$$

$$\text{WHERE } 2|B| = \frac{1}{\sqrt{5}}, \quad \alpha = 2, \quad \beta = 1$$

$$(OR) \quad f(t) = 0.4 + 0.4472 e^{-2t} \cos(t + 206.57^\circ)$$

ANOTHER EQUIVALENT ANSWER IS OBTAINED AS FOLLOWS:

$$f(t) = \frac{2}{5} + B e^{-(2-j)t} + B^* e^{-(2+j)t}, \quad \text{WHERE } B = \frac{1}{10}(-2-j)$$

$$= \frac{2}{5} + \frac{1}{10}(-2)e^{-2t}(e^{jt} + e^{-jt}) + \frac{1}{10}e^{-2t}(-je^{jt} + je^{-jt})$$

$$= \frac{2}{5} - \frac{4}{10}e^{-2t} \cos t + \frac{2}{10}e^{-2t} \sin t$$