

ESE 271

Second Exam

Name:

Spring, 2003

ID Number:

Do not place your answers on this front page.

Prob. 1 (20 points):

Prob. 2 (35 points):

Prob. 3 (25 points):

Prob. 4 (10 points):

Prob 5: (10 points):

**Prob. 1 (20 points):**

Find the single cosinusoid that is equal to

$$4 \cos(3t - 30^\circ) + 5 \sin(3t + 45^\circ)$$

$$f(t) = 4 \cos(3t - 30^\circ) + 5 \cos(3t + 45^\circ - 90^\circ)$$

$$F = 4 \angle -30^\circ + 5 \angle -45^\circ$$

$$= 4 \cos 30 - 4j \sin 30 + 5 \cos 45 - j5 \sin 45$$

$$= 3.464 - j2 + 3.536 - j3.536$$

$$= 7 - j5.536$$

$$= \sqrt{7^2 + 5.536^2} \angle \tan^{-1} \frac{-5.536}{7}$$


$$= 8.92 \angle -38.3^\circ$$

$$f(t) = 8.92 \cos(3t - 38.3^\circ)$$

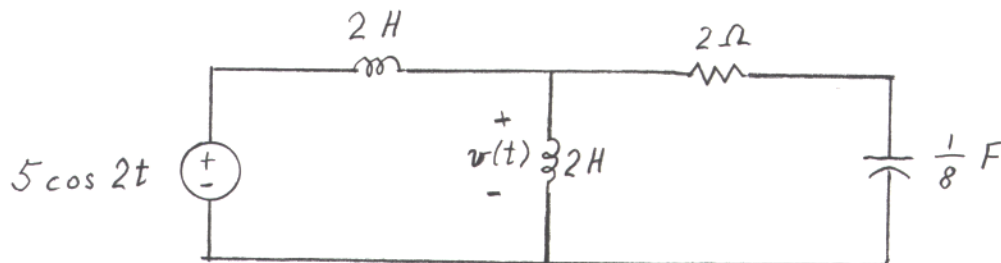
**Prob. 2 (35 points):**

Find the phasor voltage  $V$  for the sinusoid voltage  $v(t)$ .

(Your answer must be as a single complex number, but you may give it either in rectangular or polar form.)




ONE SOLUTION:

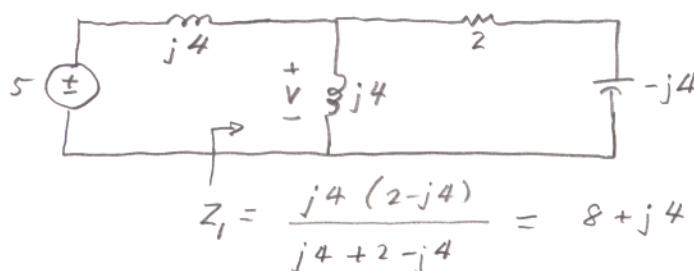

$$Z_1 = \frac{j4(2-j4)}{j4+2-j4} = 8+j4$$

$$\begin{aligned} \therefore V &= 5 \frac{Z_1}{Z_1+j4} = 5 \frac{8+j4}{8+j4+j4} = 3.75-j1.25 \\ &= 3.95 \angle -18.4^\circ \end{aligned}$$

ANOTHER SOLUTION: DO A NODAL ANALYSIS

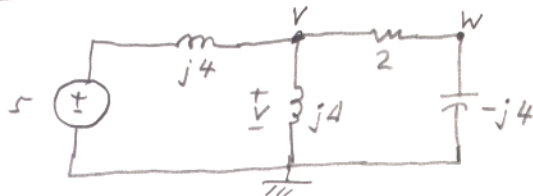

$$\frac{V-5}{j4} + \frac{V}{j4} + \frac{V-W}{2} = 0 \Rightarrow (2+j2)V - j2W = 5$$


$$\frac{W-V}{2} + \frac{W}{-j4} = 5 \Rightarrow W = \frac{-j2V}{1-j2}$$

$$(2+j2)V - j2 \frac{-j2V}{1-j2} = 0$$

$$V = 3.75-j1.25 = 3.95 \angle -18.4^\circ \quad \checkmark$$

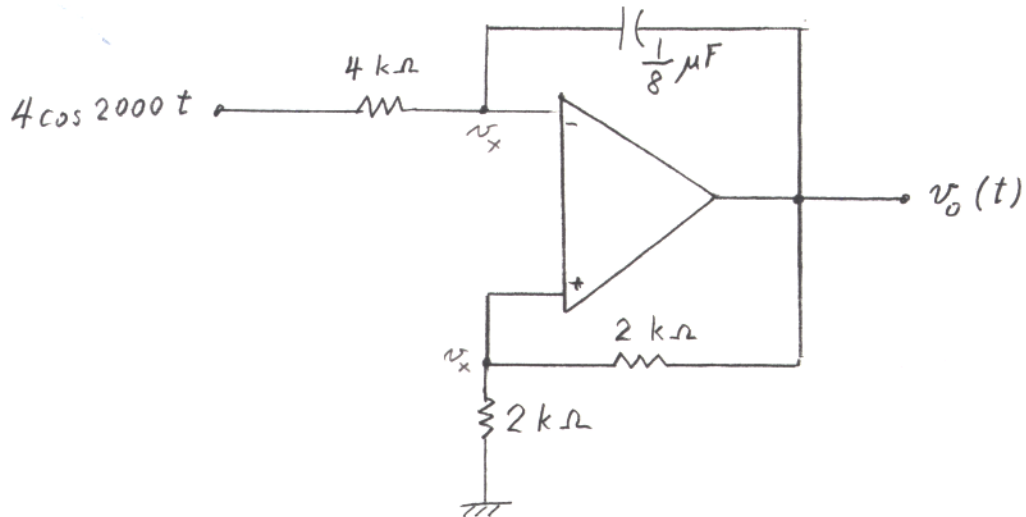**Prob. 3 (25 points):**

Find the output voltage  $v_o(t)$  as a cosinusoid.



$$\frac{1}{j\omega C} = -j \frac{1}{2000 \times \frac{1}{8} \times 10^{-6}} = -j4\text{ k}\Omega$$

$$V_x = \frac{V_o}{2}$$

$$\frac{V_x - 4}{4} + \frac{V_x - V_o}{-j4} = 0$$

$$V_x - 4 + jV_x - jV_o = 0$$

$$\frac{V_o}{2} + j\frac{V_o}{2} - jV_o = 4$$

$$V_o(1-j) = 8$$

$$V_o = 4\sqrt{2} \angle 45^\circ$$

$$v_o(t) = 4\sqrt{2} \cos(2000t + 45^\circ)$$

$$= 5.66 \cos(2000t + 45^\circ)$$

**Prob. 4 (10 points):**


Find the effective value  $I_{rms}$  for  $i(t)$ .

$$i(t) = 2 + 3 \cos(2t + 30^\circ) + 4 \cos(5t - 45^\circ)$$

$$\begin{aligned} I_{rms} &= \sqrt{2^2 + \frac{3^2}{2} + \frac{4^2}{2}} \\ &= \sqrt{16.5} \\ &= 4.06 \end{aligned}$$

Prob. 5 (10 points):

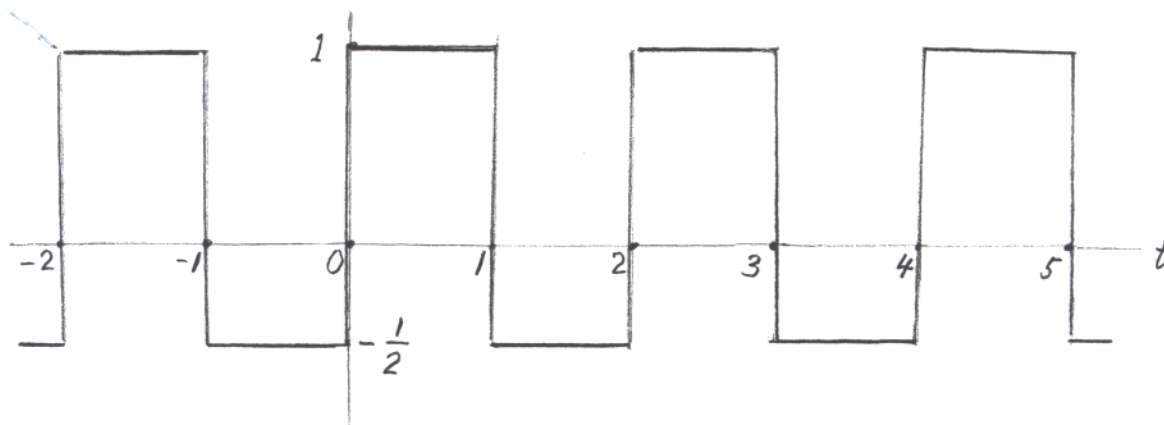Find the effective value  $I_{rms}$  for the following periodic wave.



$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt} \\ &= \sqrt{\frac{1}{2} \left( \int_0^1 1^2 dt + \int_1^2 \left(-\frac{1}{2}\right)^2 dt \right)} \\ &= \sqrt{\frac{1}{2} \left( 1 + \frac{1}{4} \right)} \\ &= .7906 \end{aligned}$$