

ESE 271

Second Exam

Name:

Fall, 2009

ID Number:

Do not place your answers on this front page.

Each problem is worth 25 points.

Prob. 1:

Prob. 2:

Prob. 3:

Prob. 4:

2nd exam

Prob. 1:

(a) (7 points) Find the single cosinusoid that equals

$$2 \sin 2t + 4 \cos(2t + 30^\circ)$$

(b) (8 points) Find the single cosinusoid whose phasor is equal to

$$2\sqrt{2}/45^\circ - 4/-60^\circ$$

(Here, $\omega = 2$ again.)

$$(a) \quad = 2 \cos(2t - 90^\circ) + 4 \cos(2t + 30^\circ)$$

$$\rightarrow 2 \angle -90^\circ + 4 \angle 30^\circ$$

$$= -j2 + 4 \cos 30^\circ + j4 \sin 30^\circ$$

$$= -j2 + 3.464 + j2$$

$$= 3.464$$

$$\rightarrow 3.464 \cos 2t$$

$$(b) \quad = 2 + j2 - 4 \cos(-60^\circ) - 4j \sin(-60^\circ)$$

$$= 2 + j2 - 2 + 4j \cdot 0.866$$

$$= j2 + j3.464$$



$$= j5.464$$

$$\rightarrow 5.464 \cos(2t + 90^\circ)$$

2nd exam

Prob. 2:

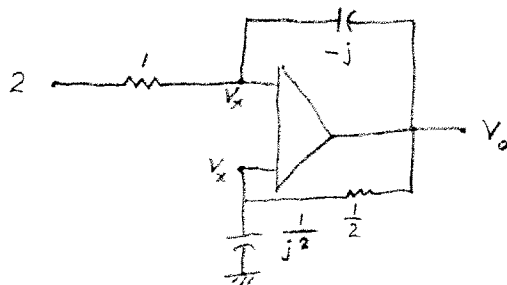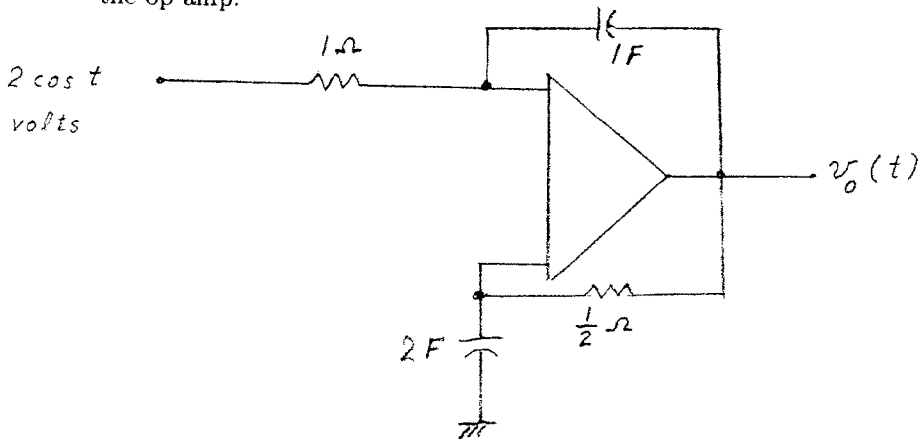Find $v_o(t)$ as a cosinusoidal function of time t . Use the virtual-short virtual-open model for the op-amp.



← The phasor circuit

At upper V_x node: $\frac{2 - V_x}{1} + \frac{V_o - V_x}{-j} = 0$

$$-(1+j)V_x + jV_o = -2$$

At lower V_x node:

$$V_x = V_o \frac{\frac{1}{j^2}}{\frac{1}{j^2} + \frac{1}{2}} = V_o \frac{1}{1+j}$$

Combine the equations:

$$-(1+j) \frac{V_o}{1+j} + jV_o = -2$$


$$V_o = \frac{2}{1-j} = \frac{2}{\sqrt{2} \angle -45^\circ} = \sqrt{2} \angle 45^\circ$$

$$v_o(t) = \sqrt{2} \cos(t + 45^\circ)$$


2nd exam

Prob. 3:

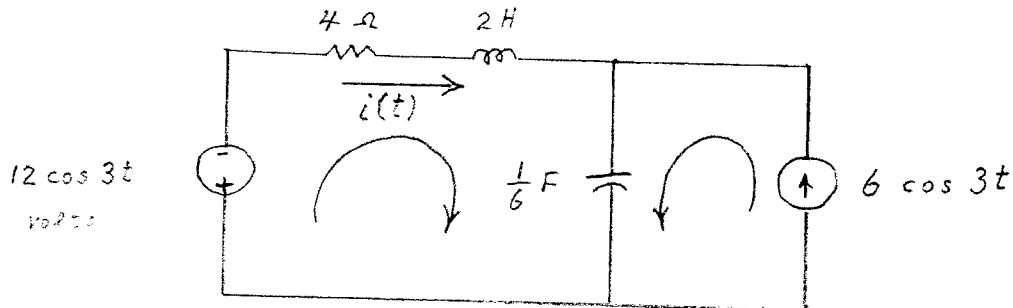Using a mesh analysis, determine the current $i(t)$ as a cosinusoid. (Warning: Be careful of the polarity of the voltage source.)



Phasor circuit:

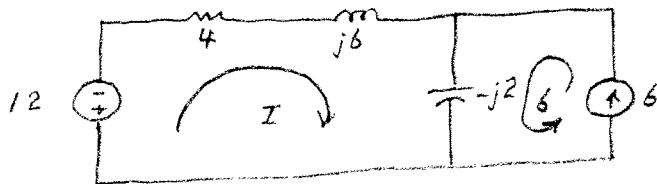

$$\text{KVL: } 12 + (4 + j6)I - j2(I + 6) = 0$$

$$I(4 + j4) = -12 + j12$$

$$I 4\sqrt{2} \angle 45^\circ = 12\sqrt{2} \angle 135^\circ$$

$$I = 3 \angle 90^\circ$$

Therefore,


$$i(t) = 3 \cos(3t + 90^\circ)$$

$$(\text{Also, } i(t) = -3 \sin 3t)$$

2nd exam


Prob. 4:

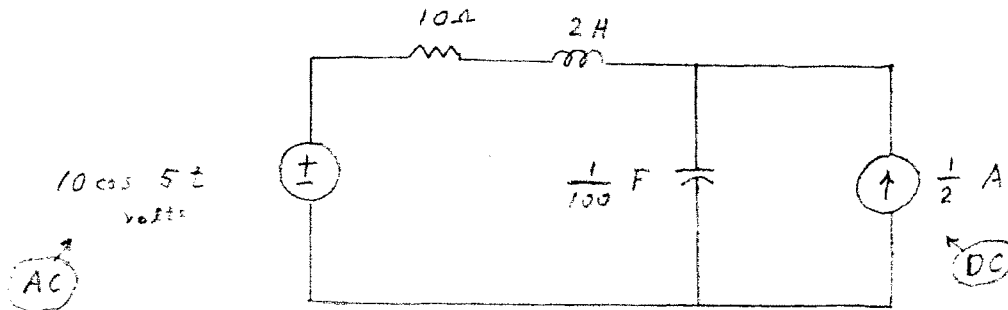What is the average power dissipated in the 10Ω resistor. The circuit is in a steady-state condition.



Use superposition:

AC source alone:

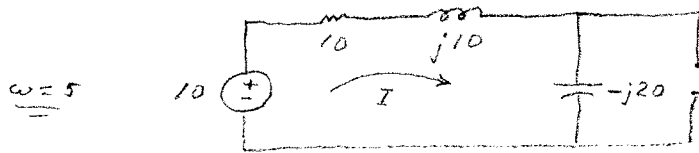


$$I = \frac{10}{10 - j10} = \frac{1}{\sqrt{2} \angle -45^\circ} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$i(t) = \frac{1}{\sqrt{2}} \cos(5t + 45^\circ)$$

$$P_{av, AC} = \frac{I_m^2 R}{2} = 2.5 \text{ W}$$

DC source alone:

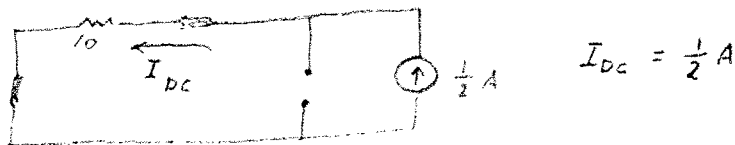

$$I_{DC} = \frac{1}{2} \text{ A}$$

$$P_{av, DC} = I_{DC}^2 R = 2.5 \text{ W}$$

Both sources acting simultaneously:

$$P_{av, total} = 5 \text{ W}$$