

ESE 271

Second Exam

Name:

Spring, 2004

ID Number:

Do not place your answers on this front page.

Every problem is worth 25 points.

Prob. 1:



Prob. 2:

Prob. 3:

Prob. 4:

Prob. 1:

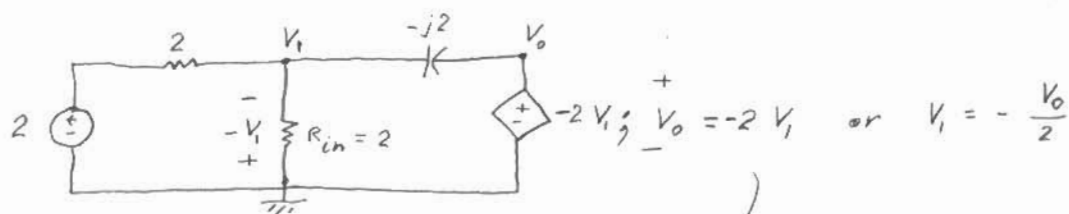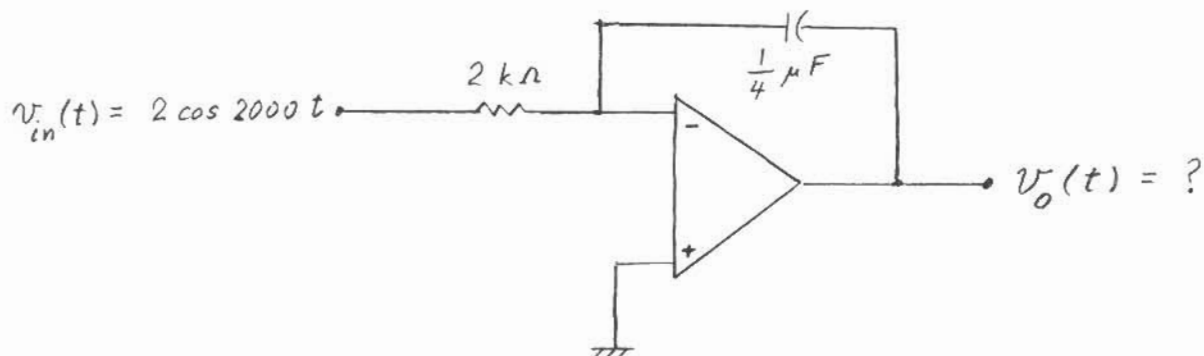Find the output voltage $v_o(t)$ as a single cosinusoid. The gain of the opamp is $A = 2$, its input resistance is $R_{in} = 2 \text{ k}\Omega$, and its output resistance is $R_o = 0$. (These are not typical values.) Do NOT use the virtual-open/virtual-short model of the opamp.



$$\frac{V_1 - 2}{2} + \frac{V_1 - V_o}{-j2} + \frac{V_1}{2} = 0$$

$$V_1(2 + j) - jV_o = 2$$

$$-\frac{V_o}{2}(2 + j) - jV_o = 2$$

$$V_o(-2 - 3j) = 4$$


$$V_o = \frac{4}{\sqrt{2^2 + 3^2} \angle \tan^{-1} \frac{-3}{-2}} = \frac{4}{3.606 \angle 180^\circ + 56.3^\circ} = 1.109 \angle -236.3^\circ = 1.109 \angle 123.7^\circ$$

So,


$$v_o(t) = 1.109 \cos(2000t - 236.3^\circ) = 1.109 \cos(2000t + 123.7^\circ)$$

Prob. 2:

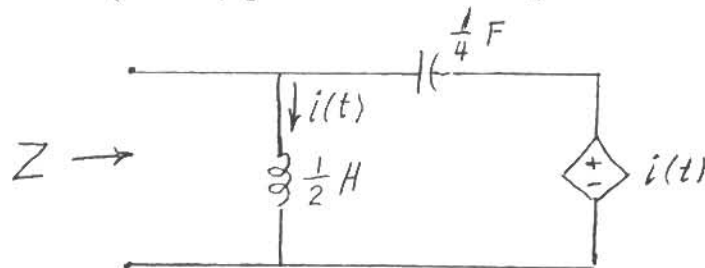Find the input impedance (i.e., the Thevenin impedance) Z of the network when the angular frequency is $\omega = 2$. (You may give Z in either rectangular form or polar form.)



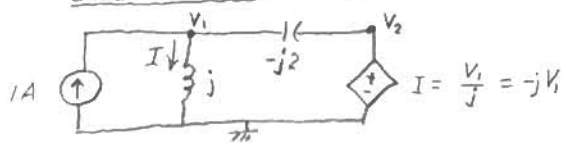ONE METHOD: APPLY A CURRENT SOURCE. DO A NODAL ANALYSIS.



At Node 1: $-1 + \frac{V_1}{j} + \frac{V_1 - V_2}{-j2} = 0 \Rightarrow V_1 + V_2 = j^2$

Also: $V_2 = -jV_1$

So: $V_1 = \frac{j^2}{1-j} = \sqrt{2} \angle 135^\circ$

Thus, $Z = \frac{V_1}{1} = \sqrt{2} \angle 135^\circ$

ANOTHER METHOD: APPLY A CURRENT SOURCE. DO A MESH ANALYSIS.




$I_1 = 1$ A. Also, around I_2 -loop: $j(I_2 - I_1) - j2 I_2 + I = 0$

$I_2(j - j2 - 1) = j - 1$

So, $V_1 = jI = j(I_1 - I_2)$

$I_2 = \frac{-1+j}{-1-j} = -j$
 $= j - jI_2 = j - 1 = \sqrt{2} \angle 135^\circ$, $Z = \frac{V_1}{1} = \sqrt{2} \angle 135^\circ$

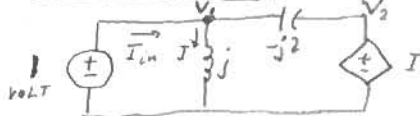ANOTHER METHOD: APPLY A VOLTAGE SOURCE. DO A NODAL ANALYSIS.




$V_1 = 1$, $V_2 = I = \frac{1}{j} = -j$

$I_{in} = I + \frac{V_1 - V_2}{-j2} = -j + \frac{1 - (-j)}{-j2} = \frac{-1-j}{2}$

$Z = \frac{1}{I_{in}} = \frac{2}{-1-j} = -1+j = \sqrt{2} \angle 135^\circ$

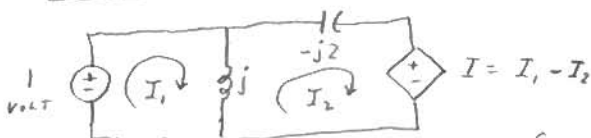ANOTHER METHOD: APPLY A VOLTAGE SOURCE. DO A MESH ANALYSIS.



$-1 + j(I_1 - I_2) = 0 \Rightarrow I_2 = j + I_1$

$j(I_2 - I_1) - j2 I_2 + I_1 - I_2 = 0 \Rightarrow I_1(1-j) + I_2(-1-j) = 0$


So, $I_1(1-j) + (j + I_1)(-1-j) = 0$

$I_1 = \frac{-1+j}{-2j}$

$Z = \frac{1}{I_1} = -1+j = \sqrt{2} \angle 135^\circ$


Prob. 3:

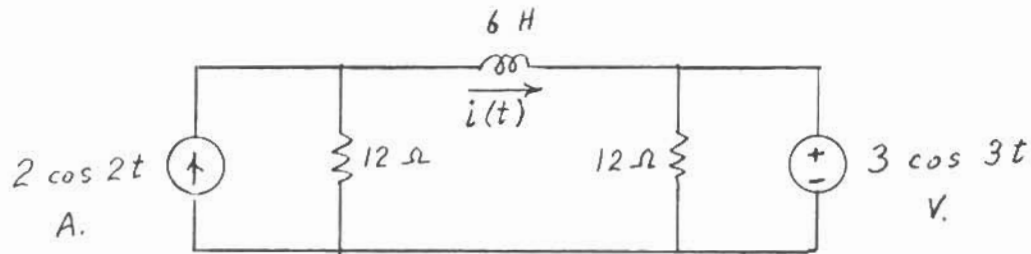Find the current $i(t)$ in the inductor as a function of time t .



WE MUST USE SUPERPOSITION:


CASE 1: THE CURRENT SOURCE ALONE.

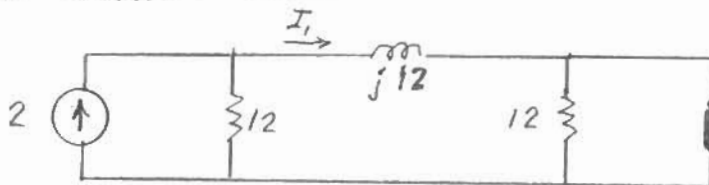

CURRENT DIVISION $\rightarrow I_1 = 2 \frac{12}{12 + j12} = 2 \cdot \frac{1}{1 + j} = \sqrt{2} \angle -45^\circ$

$$i_1(t) = \sqrt{2} \cos(2t - 45^\circ) = 1.414 \cos(2t - 45^\circ)$$

CASE 2: THE VOLTAGE SOURCE ALONE.

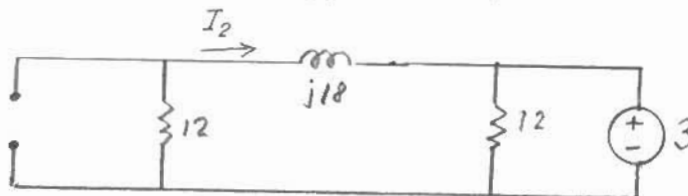

$$I_2 = -\frac{3}{12 + j18} = -\frac{1}{4 + j6} = \frac{-1}{\sqrt{4^2 + 6^2} \angle \tan^{-1} \frac{3}{2}} = .139 \angle -236.3^\circ = .139 \angle 123.7^\circ$$


$$i_2(t) = .139 \cos(3t + 123.7^\circ)$$

$$i(t) = i_1(t) + i_2(t)$$

$$= 1.414 \cos(2t - 45^\circ) + .139 \cos(3t + 123.7^\circ)$$

Prob. 4:

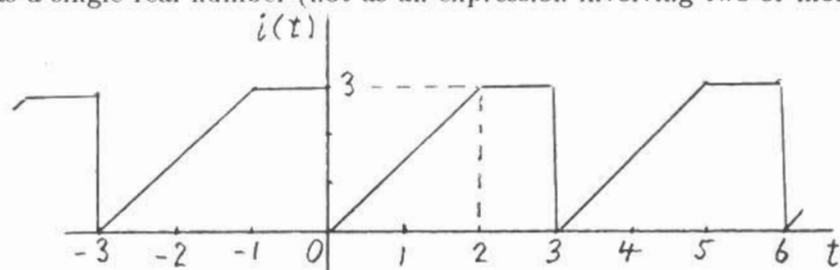Find the effective value (i.e., the rms value) of the following periodic wave. Give your answer as a single real number (not as an expression involving two or more numbers.)



$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt} \\ &= \sqrt{\frac{1}{3} \left(\int_0^2 \left(\frac{3}{2}t \right)^2 dt + \int_2^3 3^2 dt \right)} \\ &= \sqrt{\frac{1}{3} \left(\frac{9}{4} \cdot \frac{t^3}{3} \Big|_0^2 \right) + \frac{1}{3} \cdot 9} \\ &= \sqrt{\frac{1}{3} \left(\frac{9}{4} \cdot \frac{8}{3} \right) + 3} \\ &= \sqrt{2 + 3} = \sqrt{5} = 2.24 \end{aligned}$$