

ESE 271

First Exam

Name:

Spring, 2004

ID Number:

Do not place your answers on this front page.

Every problem is worth 25 points

Prob. 1:


Prob. 2:

Prob. 3:


Prob. 4:

Prob. 1:

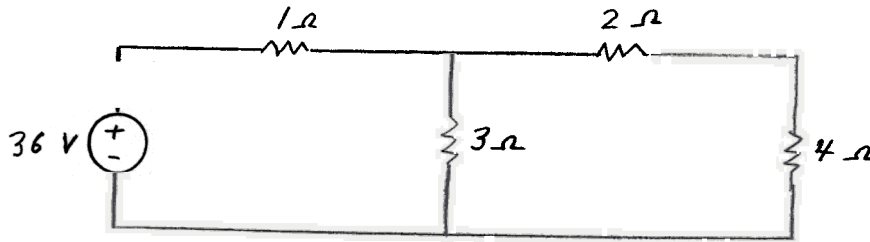Find the power dissipated in the $4\ \Omega$ resistor.



ONE METHOD: USE PROPORTIONALITY.

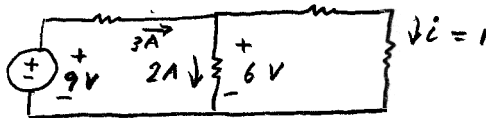


ASSUME $i = 1\text{ A}$. THEN, WE GET

$$\text{So, } i \text{ IS REALLY } i = \frac{36}{9} \times 1 = 4\text{ A}$$

$$\text{So } P_4 = 4^2 \times 4 = 64\text{ W}$$

ANOTHER METHOD: USE NODAL ANALYSIS.

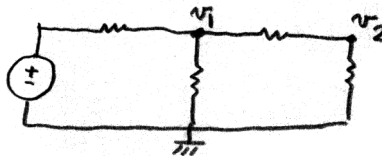

$$\left. \begin{aligned} \frac{v_1 - 36}{1} + \frac{v_1 - v_2}{2} + \frac{v_1}{3} &= 0 \\ \frac{v_2 - v_1}{2} + \frac{v_2}{4} &= 0 \end{aligned} \right\}$$

SOLVING, WE GET $v_2 = 16$

$$\text{So, } P_4 = \frac{(16)^2}{4} = 64\text{ W}$$

STILL ANOTHER METHOD: USE MESH ANALYSIS.




$$\left. \begin{aligned} i_1 + (i_1 - i_2) 3 &= 36 \\ (i_2 - i_1) 3 + 6 i_2 &= 0 \end{aligned} \right\}$$

SOLVING WE GET $i_2 = 4\text{ A}$

$$\text{So, } P_4 = 4^2 \times 4 = 64\text{ W}$$

Prob. 2:

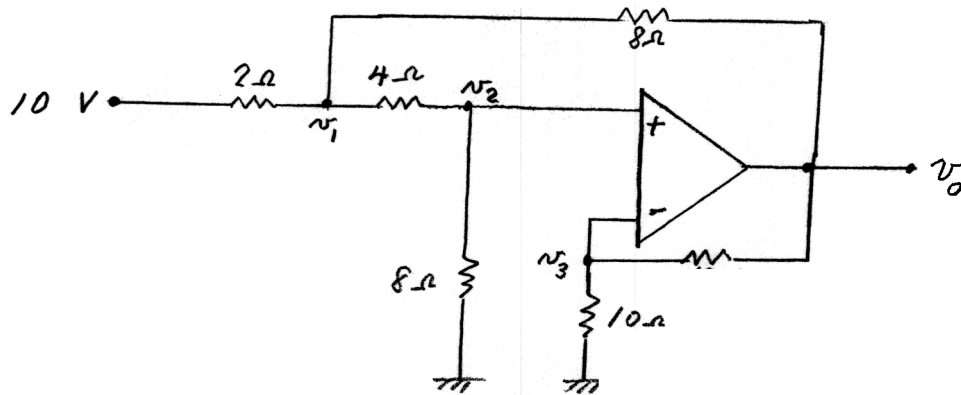Find the output voltage v_o . Use a nodal analysis with the node voltages v_o , v_1 , v_2 , v_3 .



WE MUST USE THE VIRTUAL OPEN - VIRTUAL SHORT MODEL OF THE OP AMP BECAUSE THE GAIN A IS NOT GIVEN.

$$\text{AT } v_1\text{-NODE: } \frac{10 - v_1}{2} + \frac{v_2 - v_1}{4} + \frac{v_o - v_1}{8} = 0$$

$$\text{AT } v_2\text{-NODE: } \frac{v_2 - v_1}{4} + \frac{v_2}{8} = 0$$

$$\text{AT } v_3\text{-NODE: } v_3 = v_2 = \frac{10}{10+10} v_o = \frac{v_o}{2}$$


SOLVING THESE EQUATIONS, WE GET

$$v_1 = \frac{3}{4} v_o$$

$$\text{AND } v_o = \frac{160}{13} = 12.31 \text{ V}$$

Prob. 3:

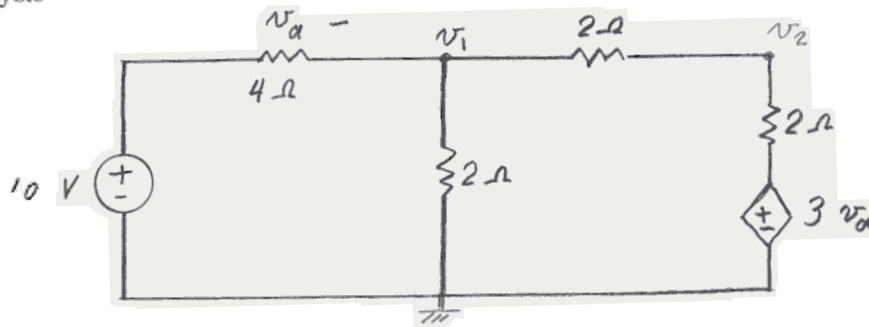In this circuit, v_1 and v_2 node voltages, and v_a branch voltage. Find v_2 . Use nodal analysis



$$v_a = 10 - v_1$$

$$5 - 3v_a = v_1$$


$$v_1 \text{ NODE} \quad \frac{v_1}{4} - \frac{v_1}{2} + \frac{v_2}{2} = 0$$

$$\text{At } v_2 \text{ NODE} \quad \frac{v_2 - v_1}{2} - \frac{v_2 - 30 + 3v_1}{2} = 0$$

$$\text{SOLVING THESE EQUATIONS} \quad \text{RE } v_2 = \frac{65}{7} = 9.2857 \text{ V}$$

Prob. 4:

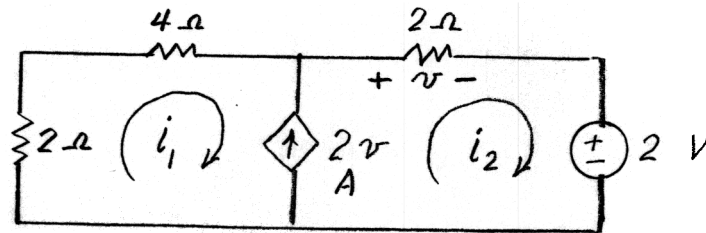Finds the branch voltage v . Do a mesh analysis using the mesh currents shown.



AT DEPENDENT CURRENT SOURCE:

$$i_2 - i_1 = 2v = 2 \times 2 i_2 = 4 i_2$$

$$\text{So } i_1 + 3 i_2 = 0$$

KVL AROUND ENTIRE CIRCUIT:

$$(2+4) i_1 + 2 i_2 + 2 = 0$$

SOLVING THESE EQUATIONS WE GET

$$i_2 = \frac{1}{8}$$

$$\text{So } v = 2 \times \frac{1}{8} = \frac{1}{4} \text{ V}$$