

ESE 271

Second Exam

Name:

Fall, 2003

ID Number:

Do not place your answers on this front page.

Prob. 1:



Prob. 2:

Prob. 3:

Prob. 4:

Prob. 1. (30 points):

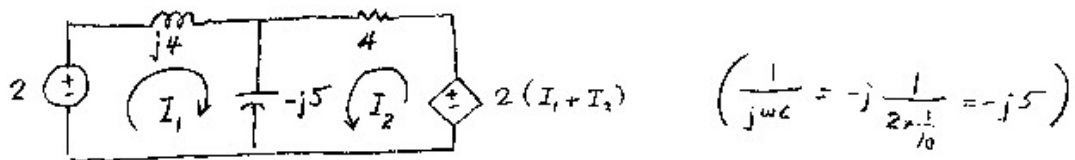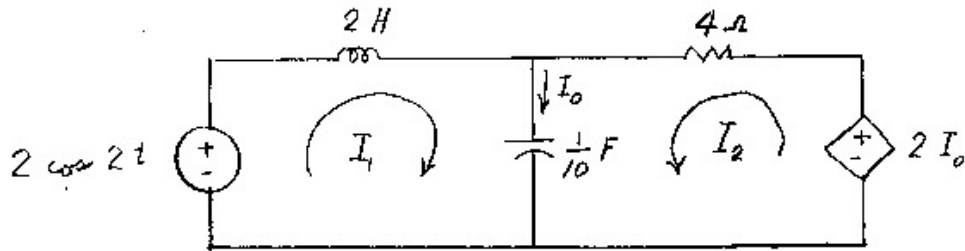Using Cramer's rule, find the phasor current I_1 as a determinant over a determinant. Do a mesh analysis using the two mesh currents I_1 and I_2 shown with their indicated directions. (The entries of the determinants should be complex numbers. Write neatly—or else points will be deducted.)



KVL FOR I_1 LOOP: $-2 + j4I_1 - j5(I_1 + I_2) = 0$

KVL FOR I_2 LOOP: $-2(I_1 + I_2) + 4I_2 - j5(I_1 + I_2) = 0$

THUS:

$$-jI_1 - j5I_2 = 2$$

$$(-2-j5)I_1 + (2-j5)I_2 = 0$$

$$jI_1 + j5I_2 = -2$$

(OR)

$$(2+j5)I_1 + (-2+j5)I_2 = 0$$

So:

$$I_1 = \frac{\begin{vmatrix} 2 & -j5 \\ 0 & 2-j5 \end{vmatrix}}{\begin{vmatrix} -j & -j5 \\ -2-j5 & 2-j5 \end{vmatrix}}$$


ANOTHER
CORRECT
ANSWER
IS \rightarrow

$$I_1 = \frac{\begin{vmatrix} -2 & j5 \\ 0 & -2+j5 \end{vmatrix}}{\begin{vmatrix} j & j5 \\ 2+j5 & -2+j5 \end{vmatrix}}$$

(THERE ARE STILL OTHER CORRECT ANSWERS.)


Prob. 2. (30 points)

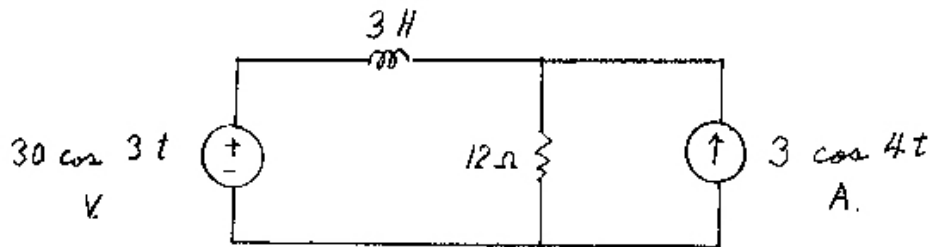Find the power P dissipated in the $12\ \Omega$ resistor.



SINCE THERE ARE DIFFERENT ω 's, WE MUST USE SUPERPOSITION:


FOR THE $30 \cos 3t$ SOURCE ALONE:

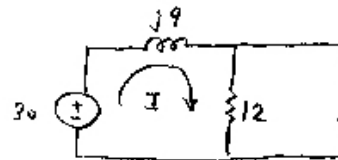

$$I = \frac{30}{12 + j9} = \frac{10}{4 + j3} = \frac{10}{5 \angle \tan^{-1} \frac{3}{4}}$$

$$|I| = 2, \quad P = \frac{|I|^2 R}{2} = \frac{4 \times 12}{2} = 24 \text{ W}$$

FOR THE $3 \cos 4t$ SOURCE ALONE:

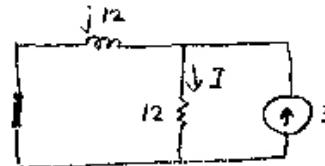


$$I = 3 \cdot \frac{j12}{12 + j12} = \frac{3j}{1 + j} = \frac{3j}{\sqrt{2} \angle 45^\circ}$$

$$|I| = \frac{3}{\sqrt{2}}, \quad P = \frac{|I|^2 R}{2} = \frac{\frac{9}{2} \times 12}{2} = 27 \text{ W}$$


THUS, TOTAL $P = 24 + 27 = 51 \text{ W}$

Prob. 3. (30 points)

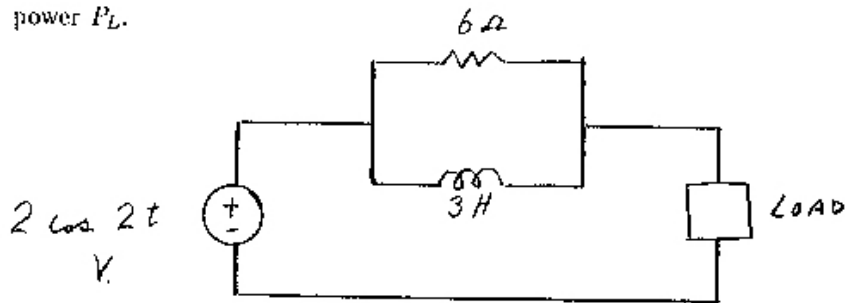In this circuit, the load is either a resistor R_L in series with an inductor L_L or a resistor R_L in series with a capacitor C_L . Find the values of R_L and of (L_L or C_L) for which the power P_L dissipated in that load is a maximum. Also, find the value of that maximum dissipated power P_L .



THE PHASOR CIRCUIT:

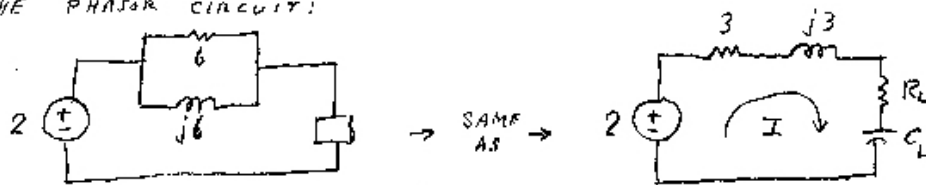

$$\frac{6(j6)}{6+j6} = \frac{j6}{1+j} \cdot \frac{1-j}{1-j} = \frac{6+j6}{2} = 3+j3. \text{ So, THE LOAD MUST HAVE A CAPACITOR } C_L$$

$$\text{THUS, } \underline{R_L = 3} \text{ AND } \underline{-j \frac{1}{2C_L} = -j3. \text{ So, } C_L = \frac{1}{6} \text{ F}}$$


THE MAXIMUM POWER DISSIPATED IS OBTAINED AS FOLLOWS:

$$I = \frac{2}{3+j3+3-j3} = \frac{2}{6} = \frac{1}{3}$$

$$\text{MAX. POWER in } R_L = \frac{|I|^2 R}{2} = \frac{\left(\frac{1}{3}\right)^2 3}{2} = \underline{\underline{\frac{1}{6} \text{ W.}}}$$

Prob. 4. (10 points)

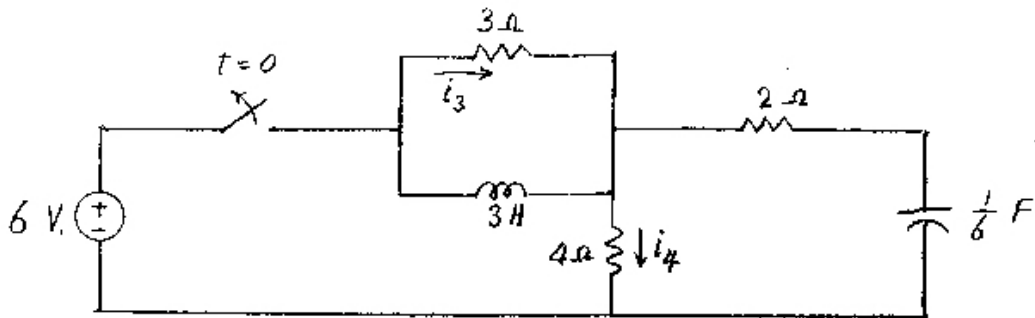
This circuit is in the DC steady state at $t = 0^-$ with the switch closed. The switch is opened at $t = 0$. For $t = 0^+$, find the current $i_3(0^+)$ flowing to the right through the $3\ \Omega$ resistor, and also find the current $i_4(0^+)$ flowing downward through the $4\ \Omega$ resistor.



At $t = 0^-$:



At $t = 0^+$:

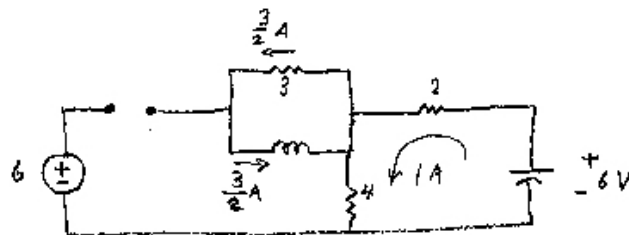

BECAUSE CURRENT IN INDUCTOR DOES NOT JUMP
AND VOLTAGE ON CAPACITOR DOES NOT JUMP,

THUS,

$$i_3(0^+) = -\frac{3}{2}\text{ A}$$

$$i_4(0^+) = 1\text{ A}$$