

ESE 271

Final Exam

Name:

Fall, 2009

ID Number:

Do not place your answers on this front page.

Each problem is worth 25 points.

Prob. 1:

Prob. 2:


Prob. 3:

Prob. 4:


final exam

Prob. 1:

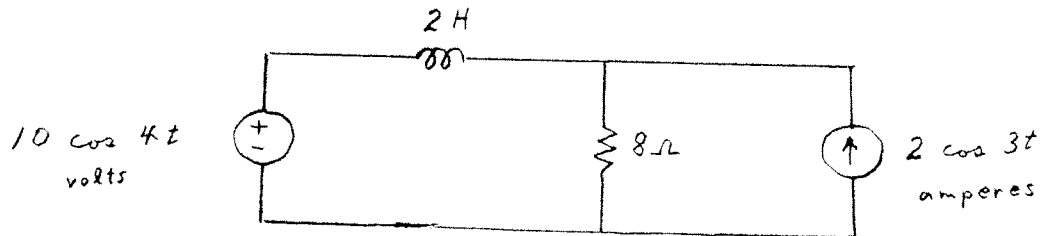This circuit is in the AC steady state. Determine the average power dissipated in the $8\ \Omega$ resistor.




FOR THE $10 \cos 4t$ SOURCE ALONE:

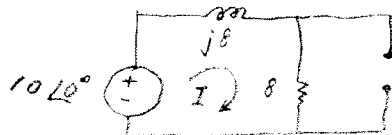

$$I = \frac{10}{8 + j8} = \frac{10}{8\sqrt{2} \angle 45^\circ}$$

$$P = \frac{|I|^2 R}{2} = \left(\frac{10}{8\sqrt{2}} \right)^2 \frac{8}{2} = 3.125 \text{ WATTS}$$

FOR THE $2 \cos 3t$ SOURCE ALONE:

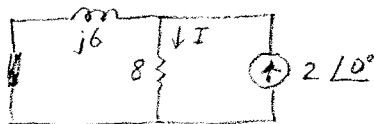

$$I = 2 \frac{j6}{8 + j6} = 2 \frac{6 \angle 90^\circ}{10 \angle 36.87^\circ}$$


$$P = \frac{|I|^2 R}{2} = \frac{(1.2)^2 8}{2} = 5.760 \text{ WATTS}$$

$$\text{TOTAL AVERAGE POWER} = 3.125 + 5.760 = 8.885 \text{ WATTS}$$


final exam

Prob. 2:

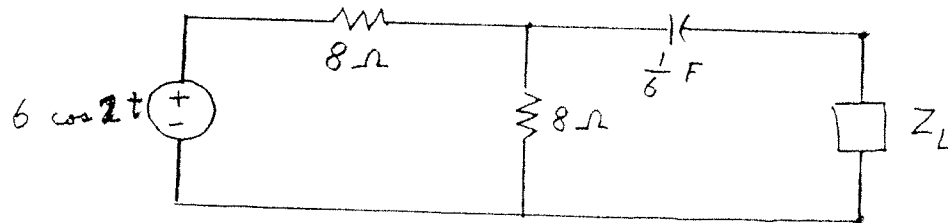
Determine Z_L so that the average power dissipated in Z_L is a maximum. Assume Z_L is a resistor in series with an inductor or capacitor. Give the value of that resistor and also of the inductor or capacitor. Also, state the value of that maximum average dissipated power.



PHASOR CIRCUIT:

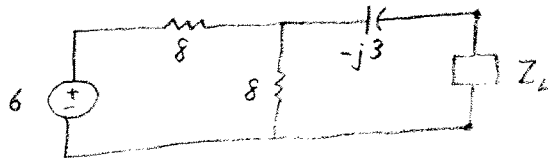

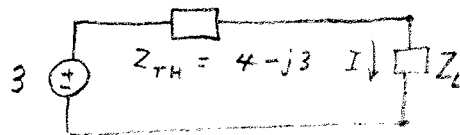THE THEVENIN EQUIVALENT CIRCUIT TO THE LEFT OF Z_L :



$$Z_{TH} = -j3 + \frac{8 \times 8}{8+8} = 4 - j3$$

THEREFORE, $Z_L = Z_{TH}^* = 4 + j3$

$$R_L = 3, \quad j\omega L = j3 \quad L = \frac{3}{2} \text{ H}$$



$$I_{MAX} = \frac{3}{4 - j3 + 4 + j3} = \frac{3}{8}$$

$$P_{AV, MAX} = \frac{I_{MAX}^2 R_L}{2} = \left(\frac{3}{8}\right)^2 \frac{4}{2} = .28125 \text{ WATTS}$$

final exam

Prob. 3:

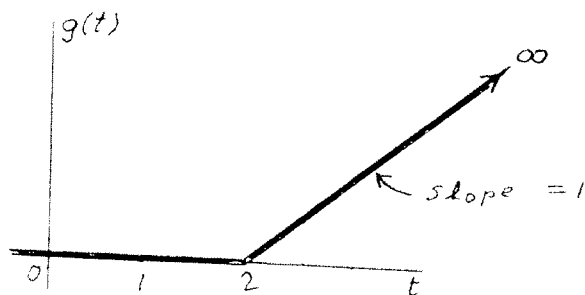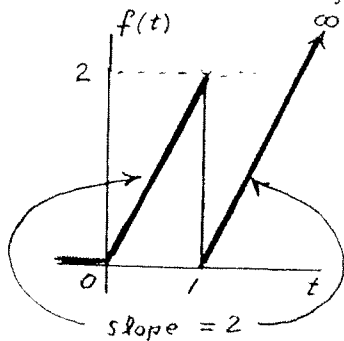Determine the convolution $f(t) * g(t)$ as a function of time t .



$$f(t) = 2r(t) - 2u(t-1)$$

$$F(s) = \frac{2}{s^2} - \frac{2}{s} e^{-s}$$

$$g(t) = r(t-2)$$

$$G(s) = \frac{1}{s^2} e^{-2s}$$

$$\begin{aligned} F(s)G(s) &= \left(\frac{2}{s^2} - \frac{2}{s} e^{-s} \right) \frac{1}{s^2} e^{-2s} \\ &= \frac{2}{s^4} e^{-2s} - \frac{2}{s^3} e^{-3s} \end{aligned}$$


$$\begin{aligned} f(t) * g(t) &= \mathcal{L}^{-1} F(s)G(s) \\ &= 2 \frac{(t-2)^3}{3!} u(t-2) - 2 \frac{(t-3)^2}{2} u(t-3) \\ &= \frac{(t-2)^3}{3} u(t-2) - (t-3)^2 u(t-3) \end{aligned}$$

final exam

Prob. 4:

In this input-output system, when the input $f(t) = u(t)$, the output $g(t) = t u(t)$.

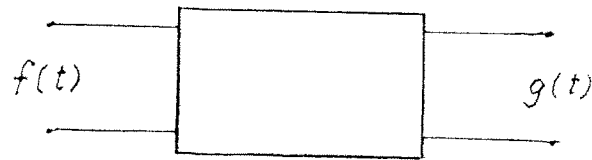Determine $f(t)$ when $g(t) = (\cos t)(u(t))$.



APPLY \mathcal{L} . IN THE FIRST CASE:

$$F(s) = \frac{1}{s}, \quad G(s) = \frac{1}{(s+1)^2}$$

THE TRANSFER FUNCTION $H(s) = \frac{G(s)}{F(s)} = \frac{s}{(s+1)^2}$

IN THE SECOND CASE:

$$G(s) = \frac{s}{s^2 + 1}$$

$$F(s) = \frac{G(s)}{H(s)} = \frac{(s+1)^2}{s^2 + 1} = \frac{s^2 + 2s + 1}{(s-j)(s+j)}$$

$$F(s) = 1 + \frac{A}{s-j} + \frac{A^*}{s+j}$$

$$A = \left. \frac{s^2 + 2s + 1}{s+j} \right|_{s=j} = 1$$

APPLY \mathcal{L}^{-1}

$$f(t) = \delta(t) + e^{jt} + e^{-jt} = \delta(t) + 2 \cos t$$